

Department of Electronic and Telecommunication Engineering

University of Moratuwa

EN4020: Advanced Digital Systems



System Bus Design and Simulation Report

Group Members:

K.G.L.P. Nawarathna	160430A
N.L.Udugampola	160640R
W.W.A.T.E.Weerasinghe	160680M

24th December 2020

Table of Contents

Table of Contents	ii
1 Introduction.....	4
2 Signal List	5
3 Functionality	7
3.1 Address Bus.....	7
3.2 Response Bus	7
3.3 WDATA Bus & RDATA Bus.....	8
3.4 Master Interface.....	9
3.5 Slave Interface.....	10
3.6 Arbiter	11
4 Arbiter Design.....	13
5 Arbiter Verification.....	15
5.1 Arbiter Testbench.....	15
5.2 Simulation Diagrams.....	16
5.2.1 Single Master Request	16
5.2.2 2 Masters Request	17
5.2.3 Split Transaction	17
5.2.4 Reset.....	17
6 Address Decoder (Slave Interface) Design.....	18
7 Address Decoder (Slave Interface) Verification.....	22
7.1 Slave Interface Testbench	22
7.2 Simulation Diagrams.....	25
7.2.1 Master write to slave (address matching)	25
7.2.2 Master read from slave (address matching)	25
7.2.3 Master is reading from slave (address is not matching)	26
7.2.4 Master is reading from slave (slave is busy).....	26
8 Top Level Verification.....	27

8.1	Top Level Testbench.....	27
8.2	Simulation Results.....	28
8.2.1	One master request.....	28
8.2.2	Two Master Request	29
8.2.3	SPLIT Transaction Viable Scenario	30
8.2.4	Reset Test.....	31
9	APPENDIX.....	32
9.1	APPENDIX A	32
9.2	APPENDIX B	32
9.3	APPENDIX C	34
9.4	APPENDIX D	35
9.5	APPENDIX E.....	40
9.6	APPENDIX F	42
9.7	APPENDIX G	47
9.8	APPENDIX H	50
9.9	APPENDIX I.....	51
9.10	APPENDIX J.....	55
9.11	APPENDIX K.....	55
9.12	APPENDIX L.....	57


1 Introduction

This document is intended to describe the design and simulation of a system bus as a partial fulfillment for the module, EN4020: Advanced Digital Systems. Required details for each of the given tasks are included in different sections of this document along with functional descriptions, IO definitions, timing diagrams, RTL & testbench codes. The design was done using Verilog. Quartus Prime and ModelSim are the software applications used for simulation and compilation for checking errors.

A system bus is a communication medium in the digital domain which facilitates data transfer between components and devices connected to it. Best example is the system bus in a computer which connects the Central Processing Unit (CPU), main memory and other major components together. Generally a system bus consists of a Data Bus to carry data, an Address Bus to determine where data should be sent and a Control Bus to maintain the proper control of the system bus without any collisions of data transfers.

In this project, we designed a custom serial system bus with a custom protocol. The design consists of a **serial address bus** with a 16-bit address format, a **serial write-data bus** to send 8-bit data to slave devices, a **serial read-data bus** to read 8-bit data from slave devices and a **response bus** for the slave devices to respond to read or write requests from master devices. There is another major component called **arbiter** which directly communicates with any master or slave device, connected to the bus in order to maintain access and control of the bus. Following diagram shows the architecture of the design.

Design Architecture

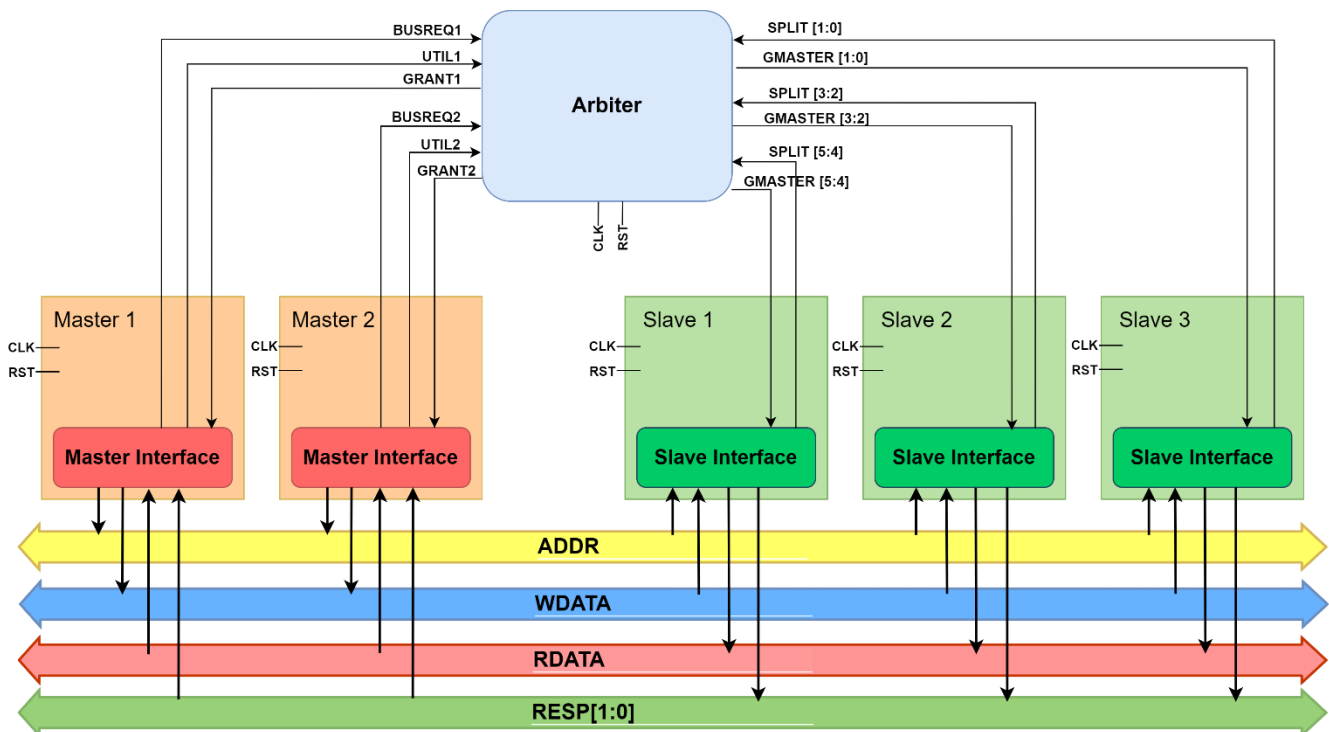

2 Signal List

The list below shows the signals in our system bus architecture, which are basically the main bus lines and the control signals, connecting with the arbiter.

Name	Source	Description
CLK Bus clock	Clock source	Bus protocol is synchronous and CLK handles all timing operations in the bus. All signal timings are related to the rising edge of CLK.
RESETn Reset	External source	Reset signal is the only asynchronous and active LOW signal. It is used to reset all the states of the system and the bus.
BUSREQx BUSREQ[1:0] for 2 masters to request bus	Master	A signal from master x to the bus arbiter which is used to inform that the master x requires the bus access. Each master has a dedicated BUSREQ signal and the arbiter facilitates up to 2 masters. When requesting the bus, master must keep this signal HIGH until it is granted access.
UTILx UTIL[1:0] for 2 masters' utilized flags	Master	If master x is utilizing the bus for a data transfer, it must keep this signal HIGH throughout the time of the transaction. The master must make UTIL signal LOW at the end of every single transaction. As a result, when the master performs a burst of many transactions, the arbiter can grant the master for each of the transactions while considering master priority as well.
GRANTx GRANT[1:0] for 2 masters' bus grant	Arbiter	This signal is made HIGH by the arbiter to indicate master x that it has permission to access the bus. Only one master will be granted at a time.
GMASTERx[1:0]	Arbiter	This signal is used by the arbiter to inform the currently granted master to slave x. If this signal is made 2'b10 , granted master is master1 and if this signal is made

GMASTER[5:0] for 3 slaves to check granted master		2'b01 , granted master is master2. In a SPLIT transaction, slave checks this signal to know when to continue.
SPLITx [1:0] SPLIT[5:0] for 3 slaves to do split requests	Slave	This signal is used by slave x to request arbiter to grant a particular master when slave x is ready to continue a previous transaction with the master to which the slave has responded BUSY in the first time. This split request can be made for the grant of master1 by making this signal 2'b10 and for the grant of master2 by making this signal 2'b01 .
ADDR Address bus	Master	This is the serial system address bus through which a granted master can send the address of a 8-bit slave register by sending a 16-bit address packet. Its first bit is a start bit which is logic 1. Next 2 bits are for the slave device address. The bit after that is for indicating whether the master is going to do a READ or a WRITE transaction. Last 12 bits are for the address of the memory location of the slave.
WDATA Data write bus	Master	This is the serial system WDATA bus used to transfer 8-bit data from the granted master to a slave during a WRITE operation.
RDATA Data read bus	Slave	This is the serial system RDATA bus used to transfer 8-bit data from a slave to the granted master during a READ operation.
RESP[1:0] Slave response bus	Slave	This is the bus used by a slave to send a response to the granted master during a transaction. There are three types of responses named as OK , BUSY , DONE which can be sent by making this bus 2'b10 , 2'b01 , 2'b11 respectively. Details of these responses are written in section 3.2


3 Functionality

3.1 Address Bus

This is the serial system address bus through which a granted master can send the address of a 8-bit slave register by sending a 16-bit address packet. It includes a start bit, the slave device address, read/write operation type and the slave memory address. When a master sends an address in the address bus, every slave connected to the bus reads 16 bits of serial data into the address decoder of slave interface (Address decoder code in [APPENDIX I](#)). After it is completed each slave decodes the address and the slave with the matching slave device address can continue the transaction. Address bus facilitates communicating with a slave device of up to 2-bit device address and up to 12-bit memory address. Connections to the address bus can be seen in the code in

[APPENDIX B](#).

Address Format

 

3.2 Response Bus

This is the bus used by a slave to send a response to the granted master during a transaction. It is a 2-bit parallel bus which only maintains two logic levels in the two electrical lines during sending a response. When the master sends an address in the address bus, the relevant slave with the matching slave device address has to respond with a OK or BUSY response to continue with the data transaction and at the end of the transaction it has to send a DONE response to indicate successful completion. These three responses are further elaborated in the below table. Connections to the response bus can be seen in the code in

[APPENDIX B](#) and the response origination occurs in the slave interface, which is in [APPENDIX I](#).

Response Types

RESP[1:0]	Type	Description
-----------	------	-------------

10	OK	OK response indicates that the address matched slave is free to start the data read/write transfer in the data bus. A data read/write transfer always happens immediately after an OK response.
01	BUSY	After the relevant slave receives the 16-bit packet sent in the address bus, the slave can reply with a BUSY response if it is not ready to receive or send data at the moment. This will lead to a split situation where the transaction is postponed, and the bus is released for other transactions of other parties.
11	DONE	After the slave sending or receiving an 8-bit data in data write/read bus, a DONE response is sent to notify the master that the transaction completed successfully.
00	NAK	Both lines in logic LOW correspond to no response.

3.3 WDATA Bus & RDATA Bus

The granted master can write 8-bit data to the address matched slave using serial WDATA bus and it can read 8-bit data from the slave using serial RDATA bus. In writing data right after the address is sent, the master must wait till it gets an OK response to start writing 8 bits of data to the WDATA bus. Also, in reading data right after the address is sent, the master must wait till it gets an OK response to start sampling the RDATA bus to receive the 8-bit data sent by the slave. WDATA and RDATA bus is capable of doing *single read, burst read, single write, burst write*. Data bus connections are in

[APPENDIX B](#) code.

SPLIT State


If the master gets a BUSY response instead of the above mentioned OK response, it must go to a SPLIT state by releasing the bus by making UTIL signal LOW, without writing anything to the WDATA BUS or sampling the RDATA bus. BUSY response is sent by the slave to the master as a way of telling that it is not ready yet and the master has to wait till the slave is not busy. In SPLIT state, the master must wait till it is granted again because of a SPLIT request made by the slave to the arbiter on behalf of the master. As soon as the master is granted again, the next response is going to be an OK response and with that the transaction can be completed using WDATA bus or RDATA bus.

Priority Control

If the bus is not utilized by any master and if there are several bus requests from several masters, the arbiter will grant the master with the highest priority and in our case, it is the master 1. This is actually very useful in burst reads and burst write.

Example: If master2 is doing a burst transaction of writing 100 of 8-bit data to slave2 and if master1 tries to read some data from slave3 when master2 is writing data in the 10th transaction of its 100 write burst, master1 will not have to wait till master2 completes 90 more transactions. Since master1 has the highest priority it will get to do its transactions after the 10th transaction of master2. Then master2 can continue its 90 remaining transactions when master1 is done.

3.4 Master Interface

 


In our system bus design, we made a separate module named master interface which can be used to connect any master device to the system bus through its master module side ports which are listed below. Its bus side ports are simply connected to the main bus lines and the dedicated control signal lines with the arbiter. Verilog code for the master interface module is in [APPENDIX G](#).

Master Module Side Ports

Port	I/O	Description
Address [15:0]	INPUT	Address of the slave for read write operations provided by the sequence in Master Core

data_out [7:0]	OUTPUT	Data received by slave is sent to Master Core from this signal
data_in [7:0]	INPUT	8-bit data which should be sent to slave provided by the sequence in Master Core
address_rdy	INPUT	Request from master core to write the provided address to the address bus
burst_en	INPUT	Become high when burst transactions are taken place
r_en	INPUT	Enable read from slave
w_en	INPUT	Enable write to slave
done	OUTPUT	When a read or write transaction completes, Master Core is notified through this signal.

3.5 Slave Interface

 


In our system bus design, we made a separate module named slave interface which can be used to connect any slave device to the system bus through its slave module side ports which are listed below. Some of its

bus side ports are connected to the main bus lines to make the slave accessible through the system bus and some are connected to the dedicated signal lines with the arbiter to make the slave capable of requesting a particular master in a split transaction while monitoring which master has access to the bus. Both of its module side and bus side ports consist of ports for address, data in and data out. As a result, this slave interface module acts as an address decoder which can be used to access any slave device with an address space up to 12bit (4k) from our system bus with a standard 16bit address format. Verilog code for the slave interface module is in [APPENDIX I](#).

Slave Module Side Ports

Signal	Source	Description
ram_address [11:0]	Slave interface	Address of the memory location inside the connected slave device (RAM).
ram_data [7:0]	Slave interface	Data which is to be written to a memory location specified by the ram_address
q [7:0]	Slave	Output data of the connected slave which represent a value stored in a memory location specified by the ram_address.
wr_en	Slave interface	Write enable signal of the connected slave.
slave_address[1:0]	Slave	Sets the device address of the connected slave. This address is used to distinguish between slave devices connected to the system bus.
slave_busy	Slave	Enable read from slave

3.6 Arbiter

 

In this system bus design, a separate module named arbiter is created. It acts as the controller for slaves and masters. The ports of arbiter are divided among masters and slaves. Arbiter accepts requests from masters, grant permission for masters to utilize the bus lines and monitor the utilization status of masters. It communicates with slaves for split transactions. Slave notifies the arbiter that they are ready for split transaction with a particular master. Arbiter informs the currently granted master to the corresponding slave, which helps slave to continue the split transaction later by contacting the arbiter. Apart from that arbiter prioritize the requests from masters when there are multiple requests. The Verilog implementation of master interface can be viewed in [APPENDIX K](#).

4 Arbiter Design

As the first step of arbiter design, it is important to understand the ports of the module.

```
1  module arbiter (
2      input clk,
3      input reset,
4      input [1:0]req_from_master,      //BUSREQ signals in format:[m1,m2]
5
6      //SPLIT signals in format:[s1->m1,s1->m2,s2->m1,s2->m2,s3->m1,s3->m2]
7      input [5:0]split_req_from_slave,
8
9      input [1:0]bus_utilization,      //UTIL signals in format:[m1,m2]
10     output reg [1:0]grant_to_master, //GRANT signals in format:[m1,m2]
11
12     //GMASTER signals in format:[s1<-m1,s1<-m2,s2<-m1,s2<-m2,s3<-m1,s3<-m2]
13     output reg [5:0]notify_granted_master_to_slave
14 ); //NOTE: m1,m2,s1,s2,s3 stands for masters and slaves
```

req_from_master indicates the requests from each master to utilize the bus line. *split_req_from_slave* refers to the request from slave to grant corresponding master. If the master is involved in memory transaction, the *bus_utilization* signal becomes high. Otherwise, it is low. Granting permission to master to write the address is accomplished by *grant_master*. Currently working master is informed to slave through *notify_granted_master_to_slave*.

In the next step the requests from masters and slaves are processed by a combinational circuit.

```
16 wire [1:0]current_requests; //[m1 requested?, m2 requested ?]
17
18 /*either get responses from masters or get request from slaves waiting in
19 the split states to grant permission for corresponding master*/
20 assign current_requests[1] = req_from_master[1] || split_req_from_slave[5]
21                             || split_req_from_slave[3] || split_req_from_slave[1];
22 assign current_requests[0] = req_from_master[0] || split_req_from_slave[4]
23                             || split_req_from_slave[2] || split_req_from_slave[0];
```

current_requests become high whenever there is a request from a master or a split request from any of the slaves to corresponding master. This signal is 2bit wide to facilitate 2 masters.

Initially no masters are granted.

```
25 // initially no master is granted. no master is notified to slave
26 initial begin
27     grant_to_master          <= 2'b00;
28     notify_granted_master_to_slave <= 6'b000000;
29 end
```

In each clock cycle the requests are processed as follows.

```
31 always @(posedge clk or negedge reset) begin
32     //asynchronous reset
33     if(~reset)begin
34         //reset to no grants and no granted notifications
35         grant_to_master          <= 2'b00;
36         notify_granted_master_to_slave <= 6'b000000;
37     end
```

```

38
39 //bus requests are checked and granted only when bus is not utilized
40 else if(bus_utilization == 2'b00) begin
41     case(current_requests) //process the requests from masters and slaves
42         ...
43         ...

```

If reset is applied, it initializes grant and notify signals. Otherwise, it checks the status of bus utilization and only grant when no master is utilized. As mentioned earlier in master interface, at the end of each memory transaction, the utilization line is released, which allows arbiter to process requests. If only master 1 is requested, grant is provided to master 1. If only master 2 is requested grant will be provided to master 2. In both instances the granted master is notified to all the slaves.

```

39 //bus requests are checked and granted only when bus is not utilized
40 else if(bus_utilization == 2'b00) begin
41     case(current_requests) //process the requests from masters and slaves
42         2'b00:begin //no requests
43             grant_to_master <= 2'b00;
44             notify_granted_master_to_slave <= 6'b000000;
45         end
46         2'b10:begin //request to grant master 1
47             //grant master 1
48             grant_to_master <= 2'b10;
49             //notify 3 slaves that master 1 is granted
50             notify_granted_master_to_slave <= 6'b101010;
51         end
52         2'b01:begin //request to grant master 2
53             //grant master 2
54             grant_to_master <= 2'b01;
55             //notify 3 slaves that master 2 is granted
56             notify_granted_master_to_slave <= 6'b010101;
57         end
58         //high priority goes to master 1
59         2'b11:begin //request to grant both master 1 and 2
60             //master 1 is granted (high priority)
61             grant_to_master <= 2'b10;
62             //notify 3 slaves that master 1 is granted
63             notify_granted_master_to_slave <= 6'b101010;
64         end
65     endcase
66 end
67 end
68
69 endmodule

```

What will happen if there is a request from both masters? In this scenario a priority-based decision should be made. Priority is given to master 1. It is depicted below.

The complete content of the arbiter.v file is given in [APPENDIX K](#).

5 Arbiter Verification

5.1 Arbiter Testbench

Below code is the testbench for the arbiter verification. With that arbiter was verified using ModelSim for following cases.

- single master request
- two master requests
- split transaction viable scenario
- reset test

arbiter_tb.v

```
1  `timescale 1ps/1ps
2  module arbiter_tb();
3
4  //TB INPUTS
5  reg clk;
6  reg reset;
7  reg [1:0] req_from_master;
8  reg [5:0] split_req_from_slave;
9  reg [1:0] bus_utilization;
10 wire [1:0] grant_to_master;
11 wire [5:0] notify_granted_master_to_slave;
12
13 //RESET
14 reg reset_release_ff1 = 1;
15 reg reset_release_ff2 = 1;
16 wire reset_with_synchronous_release;
17
18 assign reset_with_synchronous_release = reset_release_ff2 && reset;
19
20 always @(posedge clk)
21 begin
22     reset_release_ff1 <= reset;
23     reset_release_ff2 <= reset_release_ff1;
24 end
25
26 always #1 clk = ~clk;
27
28 arbiter a1(
29     .clk                      (clk),
30     .reset                    (reset_with_synchronous_release),
31     .req_from_master          (req_from_master),
32     .split_req_from_slave     (split_req_from_slave),
33     .bus_utilization          (bus_utilization),
34     .grant_to_master          (grant_to_master),
35     .notify_granted_master_to_slave(notify_granted_master_to_slave));
36
37 initial begin
38     //initially no requests from either masters or slaves
39     clk = 0;
40     reset = 1;
41     req_from_master = 2'b00;
42     split_req_from_slave = 6'b000000;
43     bus_utilization = 2'b00;
44 end
```

```


45
46 //master 2 requests from arbiter
47 #6 req_from_master = 2'b01;
48 #3 bus_utilization = 2'b01;
49 #2 req_from_master = 2'b00;
50
51 //both masters request
52 #20 req_from_master = 2'b11;
53 #6 bus_utilization = 2'b00; //bus utilization become low
54 #2 bus_utilization = 2'b10; //after 1 clock cycle utilization becomes high
55 #2 req_from_master = 2'b00;
56
57 //slave 2 sends a split request to master 2
58 #20 split_req_from_slave = 6'b000100;
59 #5 bus_utilization = 2'b00; //previous task finished
60 #2 bus_utilization = 2'b01;
61
62 //reseting the arbiter
63 #20 reset = 1'b0;
64 //inputs to arbiter from masters and slave also reset because
65 //the entire design resets at the same time
66 #2 bus_utilization = 2'b00;
67 req_from_master = 2'b00;
68 split_req_from_slave = 6'b000000;
69
70 end
71
72 endmodule

```

5.2 Simulation Diagrams

Following are the timing diagrams for the given cases extracted using ModelSim.

5.2.1 Single Master Request

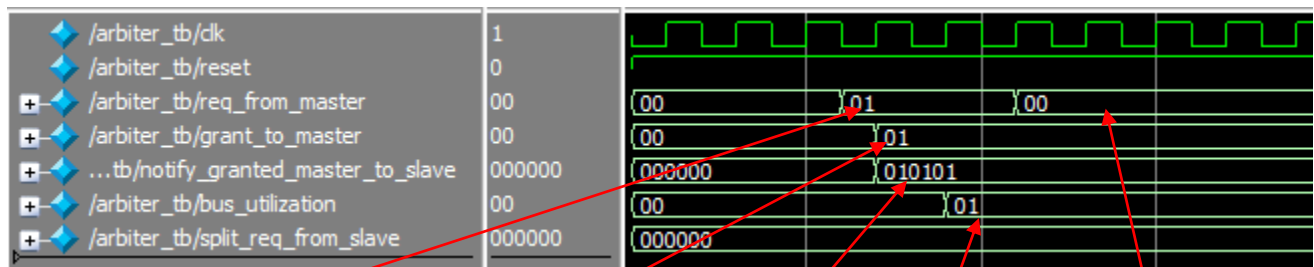

Master_2 requests


Master_2 is granted

3 slaves are informed that
Master_1 is granted

Master_1 becomes
utilized

After granted,
Master_1 stops
requesting

5.2.2 2 Masters Request

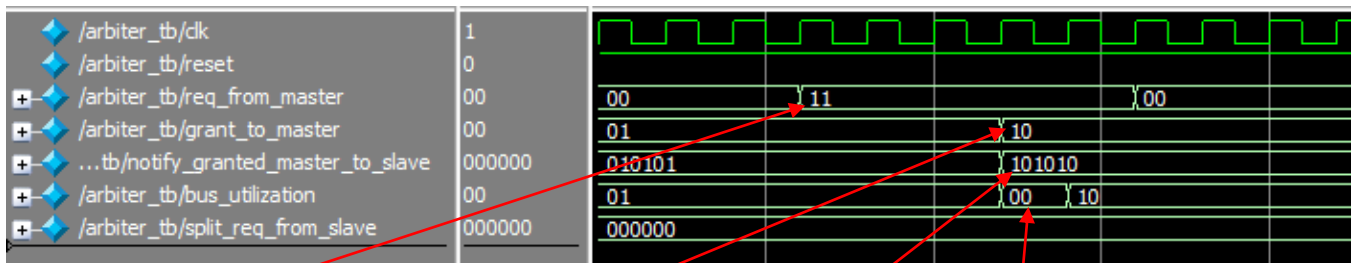


Both Masters request.
Still Master_2 is utilized.

Master_1 is granted
because of high priority

Slaves are notified that
Master_1 is granted

Master_2 completes its
task and releases util
line

5.2.3 Split Transaction

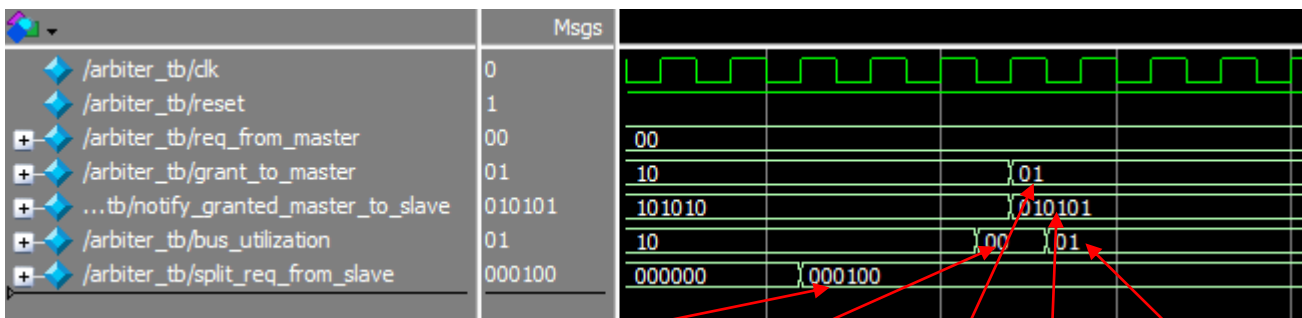

Slave_2 sends a split
request asking to activate
Master_2


Master_1
utilized signal
becomes low

Master_2 is
granted

Slaves are notified
that Master_2 is
granted

Master_2 becomes
utilized

5.2.4 Reset

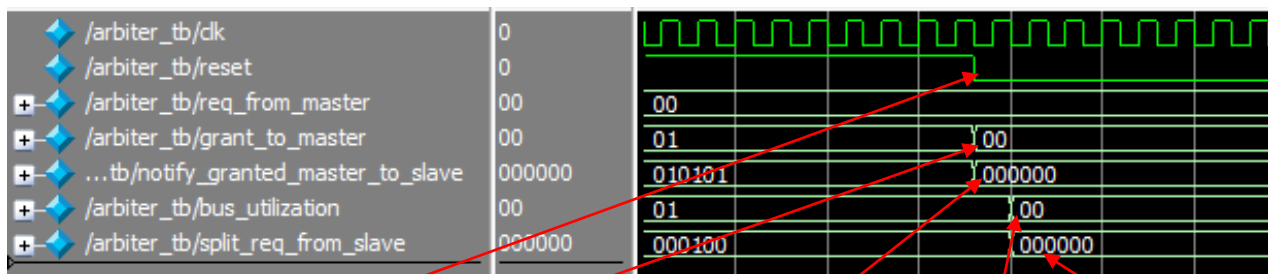

Asynchronous active
low reset is applied

No Master is granted

Slaves are
notified that no
master is granted

Utilization line
becomes low because
master interface also
resets (reset is global)

Split requests become
low because slave
interface resets

6 Address Decoder (Slave Interface) Design

The Slave interface connects the slave device (RAM) to the system bus. The address decoder for the slave interface is built inside the slave device. The purpose of the address decoder is to enable the correct slave device for a particular master request. The input and output ports of the slave interface is defined as follows. (full code for the slave_interface is in [APPENDIX D](#))

```
1  module slave_interface(  
2  
3      input wire clk,        //system clock input  
4      input wire reset,     //active low reset  
5      input wire addr,      //address bus  
6      input wire w_data,    //write data bus  
7      output wire r_data,   //read data bus  
8      output [1:0] response, //response bus  
9      output [1:0] split_request, //request split transaction  
10     input [1:0] granted_master, //indicates the active master on the bus  
11     input wire [1:0] slave_address, //sets the device address of the slave  
12     output reg slave_en, // enable signal for tri-state buffers  
13     input slave_busy,    // indicates that the slave is busy  
14     //-----for ram-----//  
15     input wire [7:0] q,   // output data from the ram  
16     output [11:0] ram_address, //address input of the ram  
17     output [7:0] ram_data, // data input to the ram  
18     output wr_en  
19 );
```

The module has number of registers to store variable data and parameters to denote constants


```
//-----PARAMETERS-----//  
21 //---STATES---//  
22 parameter AWAITING_GRANT = 4'b0000;  
23 parameter START_BIT = 4'b0001;  
24 parameter GET_ADDR = 4'b0010;  
25 parameter SEND_RESPONSE_ADDRESS = 4'b0011;  
26 parameter GET_DATA = 4'b0100 ;  
27 parameter SEND_DATA = 4'b0101 ;  
28 parameter SEND_RESPONSE_DATA = 4'b0110 ;  
29 parameter SPLIT = 4'b0111;  
30 parameter WAIT_BEFORE_GET_DATA = 4'b1000;  
31 //---RESPONSES---//  
32 parameter RESP_NAK = 2'b00;  
33 parameter RESP_BUSY = 2'b01;  
34 parameter RESP_OK = 2'b10;  
35 parameter RESP_DONE = 2'b11;
```

```
37 //-----REGISTERS-----//  
38 reg [3:0] state = START_BIT;  
39  
40 reg [15:0] r_addr = 0;  
41 reg [7:0] r_data_in = 0;  
42 reg r_data_out = 0;  
43 reg [1:0] r_response = 0;  
44 reg [1:0] r_split = 0;  
45 reg [4:0] addr_count = 0;  
46 reg [3:0] data_count = 0;  
47 reg wr_en_bit = 0;  
48 reg [15:0] split_address = 0;  
49 reg [1:0] split_master = 0;  
50 reg [1:0] r_split_request = 0;  
51 reg [3:0] busy_count = 5;
```

The Slave interface clocks from the main system clock and it has an asynchronous active low reset which sets all registers to their default values. The module functions as a state machine with 9 states. The names and functionality of each state is described in the following diagram.

STATE	Value	Description
START_BIT	0001	Default state of the module. During this state, the address bus is continuously checked for the start condition. (start bit)
GET_ADDR	0010	15-bit address which follows the start bit is captured during this state.
SEND_RESPONSE _ADDRESS	0011	Decode the 2-bit slave device address, r/w bit and the 12-bit slave memory address. Responds accordingly to the master if the device address is matching.
GET_DATA	0100	Capture the 8-bit data from the master.
SEND_DATA	0101	Send 8-bit data to the master.
SEND_RESPONSE _DATA	0110	Respond accordingly to the master after the transaction is complete.
SPLIT	0111	Slave is currently busy. Wait until the slave becomes active again.
WAIT_BEFORE_ GET_DATA	1000	Wait one clock cycle before capturing data from the W_DATA bus.
AWAITING_GRANT	0000	After issuing a split transfer request, wait until the arbiter grants permission to transfer.

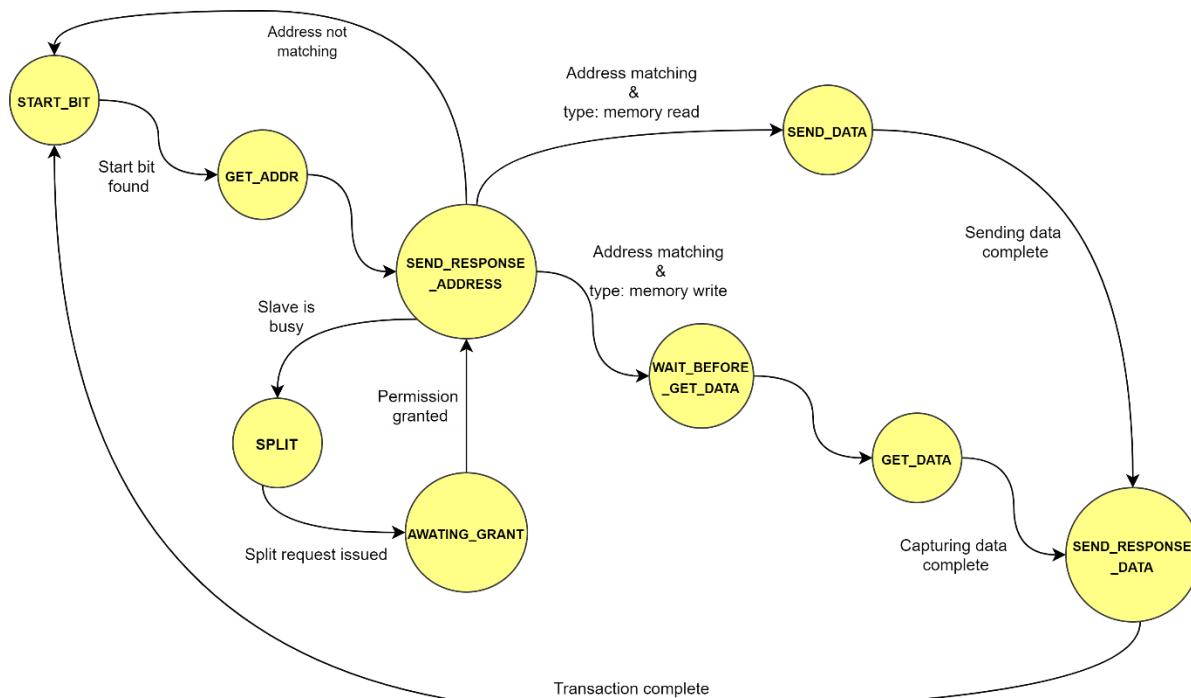The following diagram shows the transitions between states.



Address Decoder

The address decoder inside the slave interface modules serve three purposes.

- Detect the start bit
- Capture the 15-bit address
- Decode the slave device address, slave memory address and identify the type of transaction.

Since the backbone of the slave interface module is a finite state machine, the above three functions of the address decoder is implemented in the START_BIT, GET_ADDR_ and SEND_RESPONSE_ADDRESS states respectively.

```
77 // This is the default state of the module
78 // identifies the start bit of the address
79     START_BIT: begin
80         slave_en <= 0;
81         if (addr==1) begin
82             state <= GET_ADDR;
83             addr_count<=14;
84             wr_en_bit<=0;
85             r_addr<=0;
86             r_data_in<=0;
87             r_data_out<=0;
88         end
89         else
90             state <= START_BIT;
91
92         addr_count<=15;
93         r_response<=RESP_NAK;
94     end
```

The START_BIT state is the default state of the slave interface module. During this state, the module continuously checks the address bus to detect its transition from logic 0 to logic 1 which is the start bit. After successfully detecting a start bit, the slave interface changes its state to GET_ADDR.

```
95 //Capturs the 15-bit address which follows the
start bit
96     GET_ADDR: begin
97
98         if (addr_count>1) begin
99             r_addr[15:0] <= {r_addr[14:0],addr};
100             addr_count <= addr_count -1;
101             state <= GET_ADDR;
102         end else begin
103             r_addr[15:0] <= {r_addr[14:0],addr};
104             state <= SEND_RESPONSE_ADDRESS;
105         end
106         wr_en_bit<=0;
107         r_response<=RESP_NAK;
108     end
```

During the GET_ADDR state the slave interface samples the address bus at each positive clock edge to capture the 15-bit address which immediately comes after a start bit. After successfully capturing the address the module changes its state to SEND_RESPONSE_ADDRESS.

```

110 //decode the slave address and the type of
transaction (mem r/w)
111 //and send the appropriate response to the
master.
112     SEND_RESPONSE_ADDRESS: begin
113     // check for slave address
114     if (r_addr[14:13] == slave_address) begin
115         slave_en <= 1;
116
117         if(slave_busy == 0)begin
118             if (r_addr[12]==1) begin
119                 // do this for mem write
120                 state<= WAIT_BEFORE_GET_DATA;
121                 r_response<=RESP_OK;
122                 data_count<=8;
123             end
124             else begin// for mem read
125                 state<= SEND_OK;
126                 r_response<=RESP_DONE;
127                 data_count<=7;
128             end
129         else begin
130             r_response<=RESP_BUSY;
131             // send BUSY response
132             split_address<= r_addr;
133             split_master<= granted_master;
134             state <= SPLIT;
135         end
136     else begin
137         state<=START_BIT;
138     end
139 end

```

During the SEND_RESPONSE_ADDRESS state the module decodes the 15-bit address which was successfully captured during the previous state. The module first checks the 15th and 14th bits of the captured address which represent the slave device address of the master request against the actual slave device address. If the slave device address is not matching it change its state to START_BIT which is the idle state of the slave interface. If the device address is matching, then the module checks if the slave is busy. If the slave is busy, then a BUSY response is sent back to the master and the module changes its state to SPLIT. Otherwise the module checks the type of the transaction. If the transaction is a memory write type, then it issues an OK response and move to the WAIT_BEFORE_GET_DATA state. If it is a memory read type transaction the slave interface issues an OK response and move to the GET_DATA state.

7 Address Decoder (Slave Interface) Verification

7.1 Slave Interface Testbench

```
1  `timescale 1ps/1ps
2  module slave_top();
3  //-----TB_INPUTS-----//
4  reg clock50;
5  reg reset;
6  reg address_bus;
7  reg w_data_bus;
8  reg [1:0] slave_address;
9  reg [1:0] granted_master;
10 reg slave_busy;
11
12 //-----TB_OUTPUTS-----//
13 wire r_data_bus;
14 wire [1:0] split_request;
15 wire [1:0] response_bus;
16
17 //-----INTERNAL_WIRE-----//
18 wire [7:0] q;
19 wire [11:0] ram_address;
20 wire [7:0] ram_data;
21 wire wr_en;
22 wire      sibufin_r_data_bus;
23 wire [1:0] sibufin_response_bus;
24 wire      sibufin_en;
25 //-----Tristate Buffers for RDATA,RESPONSE bus-----//
26 bufif1 buf_r_data_bus(r_data_bus, sibufin_r_data_bus, sibufin_en);
27 bufif1 buf_response_bus1(response_bus[1], sibufin_response_bus[1], sibufin_en);
28 bufif1 buf_response_bus0(response_bus[0], sibufin_response_bus[0], sibufin_en);
29
30 //-----SLAVE_INTERFACE INSTANTIATION-----//
31 slave_interface SLAVE(
32     .clk          (clock50),
33     .reset        (reset),
34     .addr         (address_bus),
35     .w_data       (w_data_bus),
36     .r_data       (sibufin_r_data_bus),
37     .response     (sibufin_response_bus),
38     .split_request (split_request),
39     .slave_address (slave_address),
40     .granted_master (granted_master),
41     .q            (q),
42     .ram_address  (ram_address),
43     .ram_data     (ram_data),
44     .wr_en       (wr_en),
45     .slave_en     (sibufin_en),
46     .slave_busy   (slave_busy)
47 );
48
49 //-----RAM_INSTANCE-----//
50 syncRAM RAM_BASIC(
51     .dataOut      (q),
52     .dataIn       (ram_data),
53     .Clk          (clock50),
54     .Addr         (ram_address),
```

```

55     .Wr_en          (wr_en),
56     .reset          (reset)
57 );
58
59 reg reset_release_ff1 = 1;
60 reg reset_release_ff2 = 1;
61 wire reset_with_synchronous_release;
62
63 assign reset_with_synchronous_release = reset_release_ff2 && reset;
64
65 always @(posedge clock50)
66 begin
67     reset_release_ff1 <= reset;
68     reset_release_ff2 <= reset_release_ff1;
69 end
70
71
72 reg[15:0] address;
73 reg[7:0] data;
74 integer i;
75 always #1 clock50 = ~clock50;
76
77 //---TEST_INPUTS
78
79 initial begin
80
81 //---SET THE INITIAL CONDITIONS
82 clock50=1'b0;
83 reset =1'b1;
84 address_bus=1'b0;
85 w_data_bus=1'b0;
86 slave_address=2'b01;
87 slave_busy=1'b0;
88 granted_master=2'b01;
89 address = {1'b1,2'b01,1'b1,12'b001110001010};
90 data=8'b10001010;
91
92 //--- master 01 is writing data to slave 01-----//
93 //--- sending address
94 #2;
95 reset=0;
96 #2;reset=1;
97
98 #1;
99 for (i=0;i<16;i=i+1) begin
100     address_bus=address[15-i]; #2;
101     end
102 #4;
103
104 //---sending data
105 for (i=0;i<8;i=i+1) begin
106     w_data_bus=data[7-i]; #2;
107     end
108 //-----transaction done-----//
109 #16;
110 //--- master 01 is reading from slave 01-----//
111 address = {1'b1,2'b01,1'b0,12'b001110001010};
112 //--- sending address
113 for (i=0;i<16;i=i+1) begin
114     address_bus=address[15-i]; #2;
115     end

```

```

116 #28;
117 //-----transaction done-----//
118
119 //--- master 01 reading from slave 11----- -//
120 address = {1'b1,2'b11,1'b0,12'b001110001010};
121 //--- sending address
122 for (i=0;i<16;i=i+1) begin
123     address_bus=address[15-i]; #2;
124     end
125 #10;
126
127 //-----transaction done-----//
128
129 //--- master 01 reading from slave 01----- -//
130 //--- but the slave 01 is busy -----//
131 //--- sending address
132 address = {1'b1,2'b01,1'b0,12'b001110001010};
133 slave_busy=1;
134 for (i=0;i<16;i=i+1) begin
135     address_bus=address[15-i]; #2;
136     end
137 #5;
138 //--- arbiter release the master
139 granted_master=2'b00;
140 #5;
141 //--- slave become active after 10 clock periods
142 slave_busy=0;
143 #3;
144 //--- arbiter grant master 01
145 granted_master=2'b01;
146 //-----transaction done-----//
147 end
148 endmodule


```


7.2 Simulation Diagrams

Following are screenshots extracted from the full timing diagram taken using ModelSim.

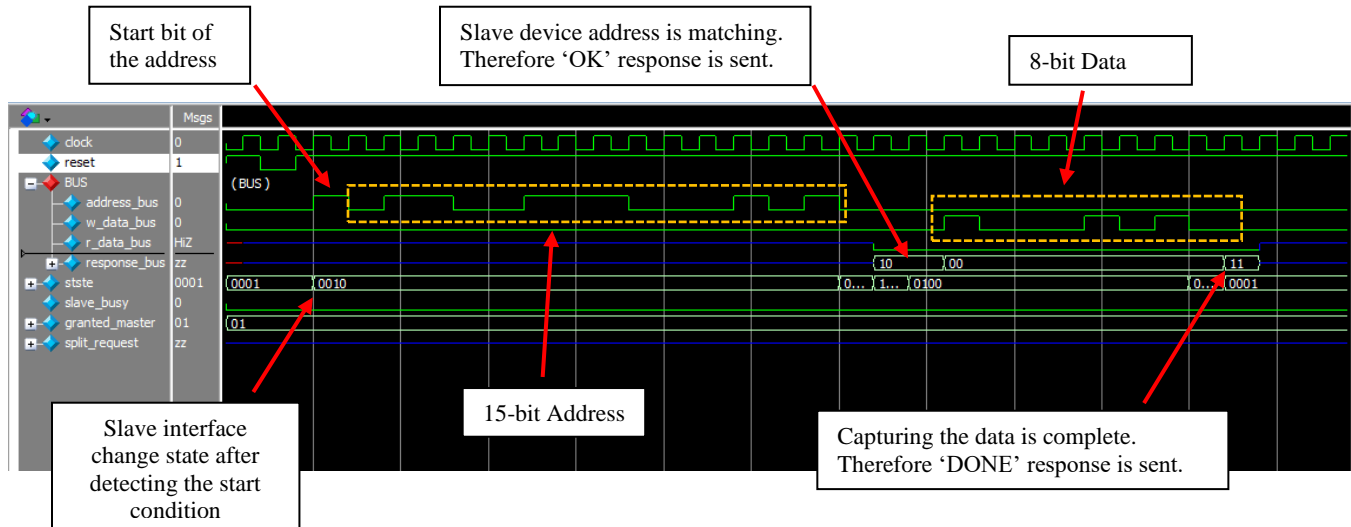
7.2.1 Master write to slave (address matching)

In the following diagram the master 01 is writing a byte of data (10001010) to the memory address 001110001010 of the slave device with device id '01'.



 
7.2.2 Master read from slave (address matching)

In the following diagram, the master 01 is reading a byte of the data from the slave memory address 001110001010. This is the same memory location where the master 01 wrote 10001010 in the first transaction. Therefore, the slave is expected to send 10001010 in the *r_data_bus*.



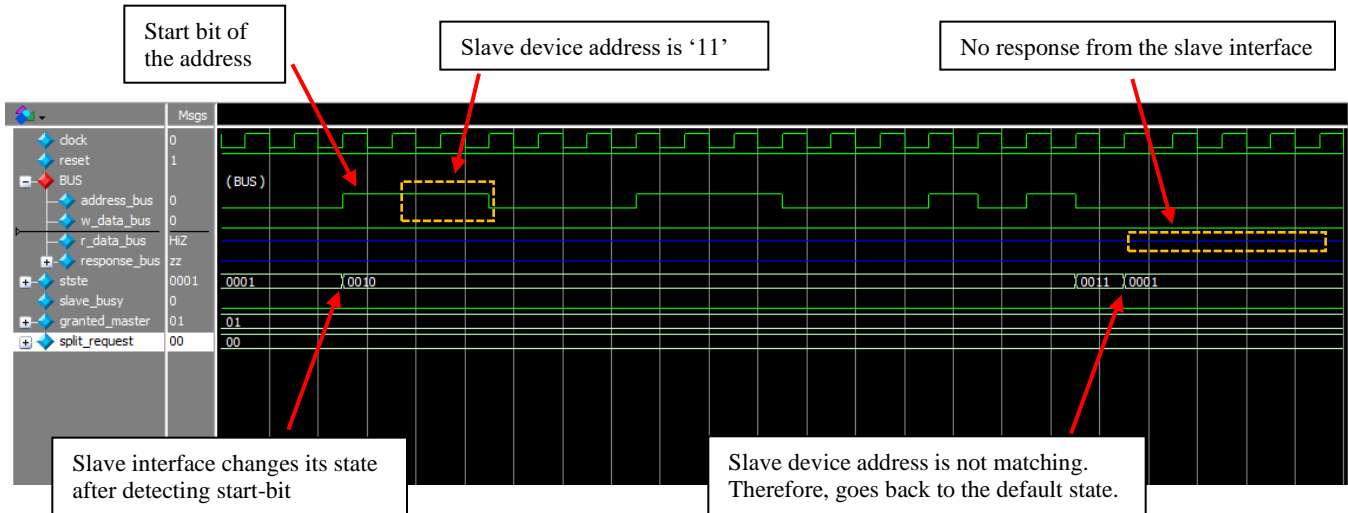
7.2.3 Master is reading from slave (address is not matching)

The following diagram demonstrate a scenario where master 01 is trying to read 8-bit data from slave with device address '11' but such slave does not exist on the bus. The slave devices with different device addresses are expected to not to respond to such a master request.



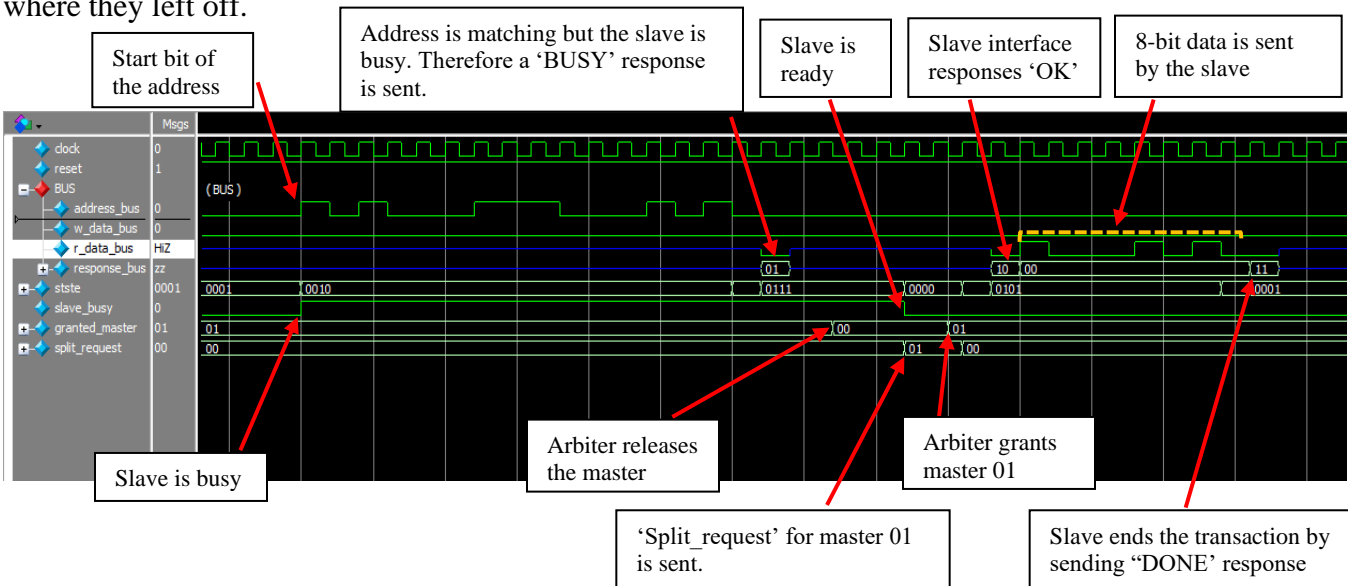
7.2.4 Master is reading from slave (slave is busy)

The following diagram shows a scenario where master 01 is trying to read from slave 01 but the slave is busy and cannot continue the transaction. In such cases, the slave is expected to issue a 'BUSY' response and the master will release the bus. Once the slave is ready, the slave interface will request a split transaction from the arbiter. Once the arbiter grants permission to the master, they will continue from where they left off.



8 Top Level Verification

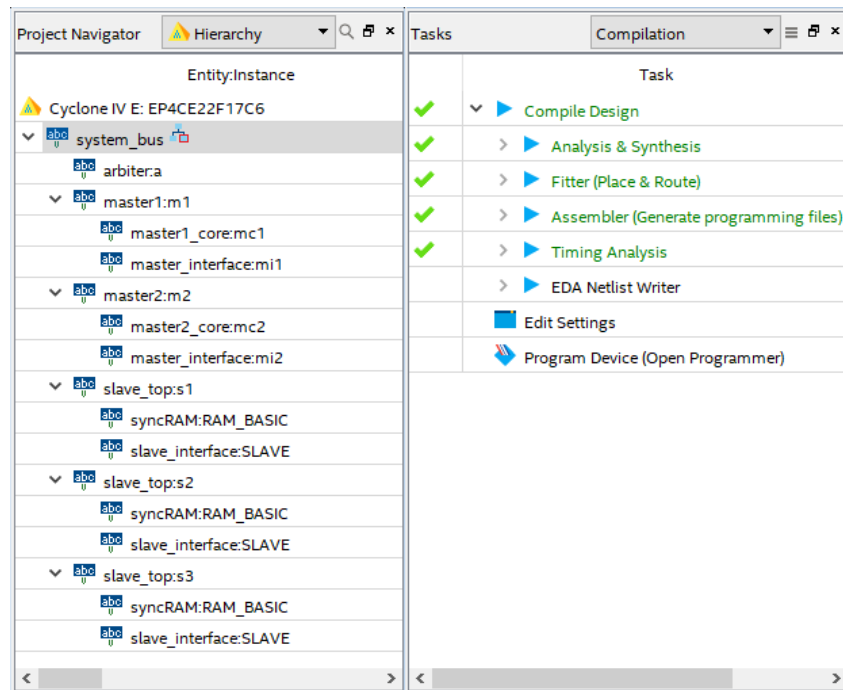In the final stage we integrated all the separately verified components into a final complete bus design with two masters with master1 having high priority and three slaves with 2k, 2k, 4k memory spaces. Following is the hierarchy of the design.



8.1 Top Level Testbench

```
1  module system_bus_tb;
2
3  //Only input variables from tb to the design are clock and reset
4  reg clk      = 0;
5  reg reset    = 0;
6
7  //asynchronous reset with a 2-flop synchronizer
8  reg reset_release_ff1 = 0;
9  reg reset_release_ff2 = 0;
10 wire reset_with_synchronous_release;
11 assign reset_with_synchronous_release = reset_release_ff2 && reset;
12
13 always @(posedge clk)begin
14     reset_release_ff1 <= reset;
15     reset_release_ff2 <= reset_release_ff1;
16 end
17
18 //Initially the design is in reset state
19 initial begin
20     clk = 0;
21     #25 reset = 1; //Releasing the initial reset
22     #10281 reset = 0; //Reset test in the middle
23     #28 reset = 1; //Releasing reset in the reset test
24 end
```

```

25
26 //Clock signal generation
27 always #10 clk = ~clk;
28
29 //System Bus Instantiation
30 system_bus sb(
31     .clk      (clk),
32     .reset    (reset_with_synchronous_release)
33 );
34
35 endmodule

```

Testbench for the final bus design is very small because all the operations are handled in the master cores themselves. Only the clock and the reset signals were given to the system bus design.


Each master interface is attached to a master core and their flow of operation of is a predefined set of read, write tasks, and idle times. ([APPENDIX C](#) shows how these 2 are interfaced together). Codes of the master1 and master2 cores, used for the top-level verification are in [APPENDIX D](#) and [APPENDIX E](#).

8.2 Simulation Results

Following are screenshots extracted from the full timing diagram taken using ModelSim.


8.2.1 One master request

READ Operation

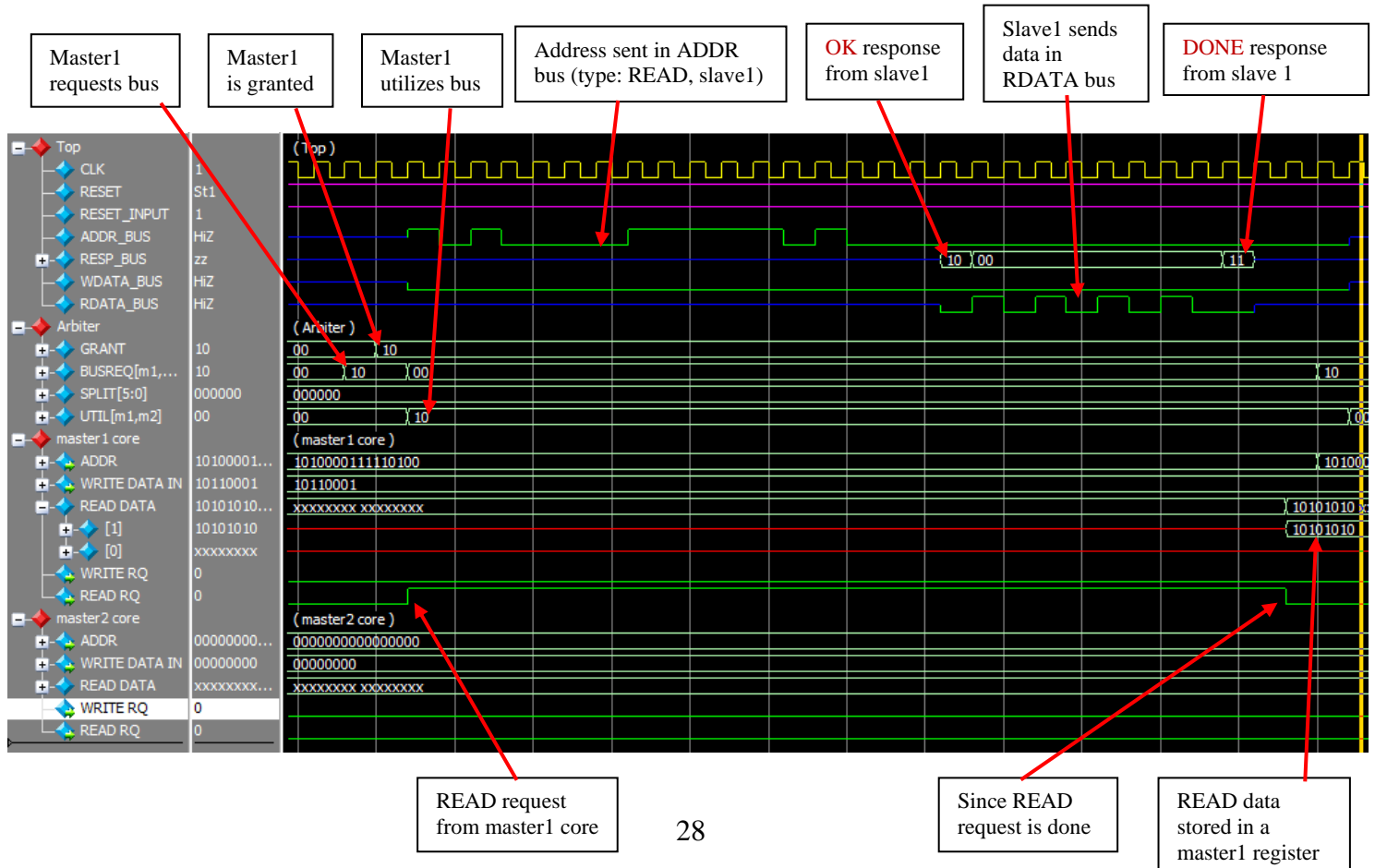

In the above scenario the address sent in the address bus is 1010000111110100. There the slave device address is 01 (slave 1), transfer type bit is 0 (READ transfer) and the slave memory address is 500. Therefore, master 1 is reading the 500th memory location of slave1 and storing it in a register in master1.

 
WRITE Operation (with a SPLIT viable scenario)



 
8.2.2 Two Master Request

If there are two bus requests from both masters, the moment the bus becomes unutilized, master1 will be granted because it has the highest priority. This can be easily observed when one master requesting the bus while the other master is doing a burst transaction. Following are such cases.


Master2 requesting while master1 in doing a burst



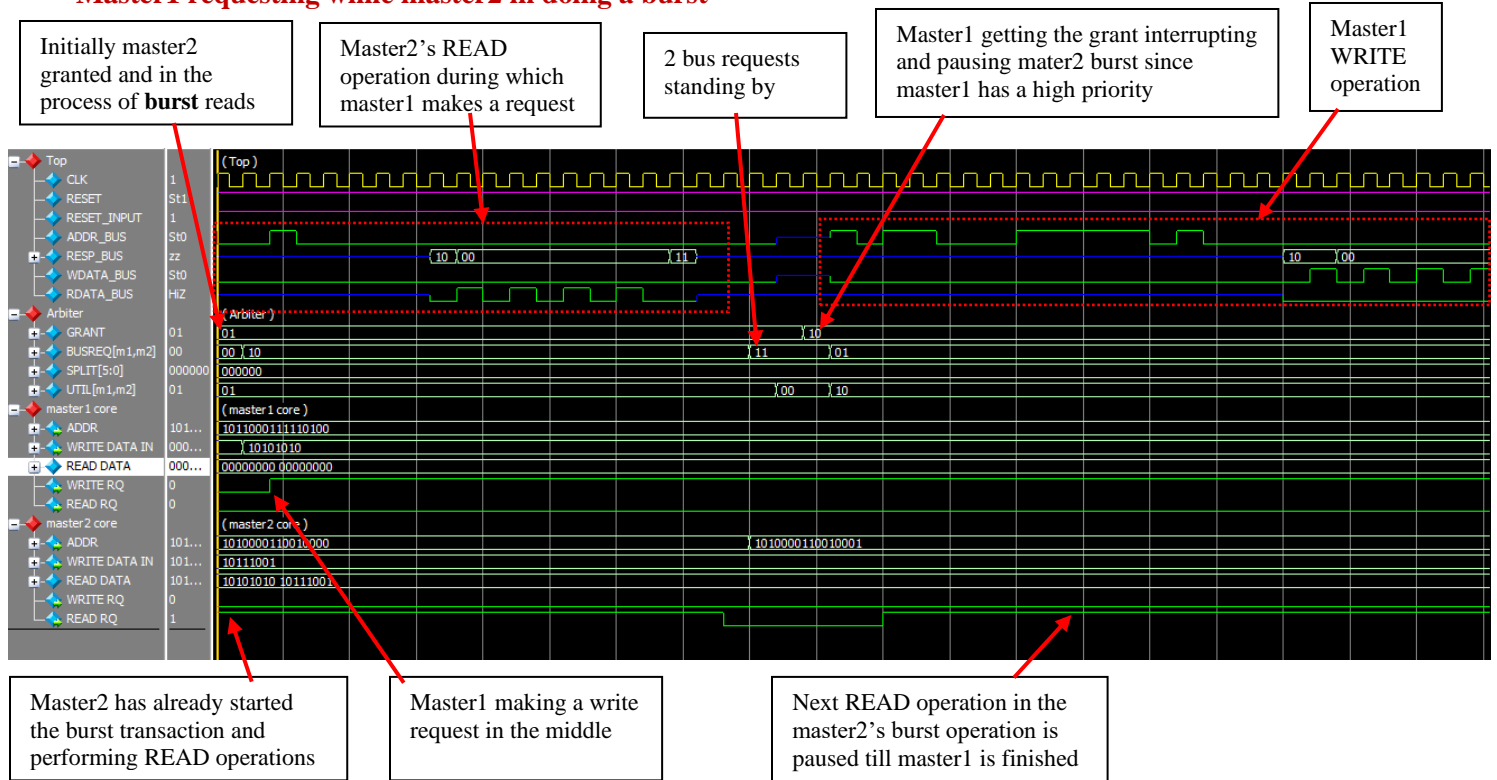Master1 requesting while master2 in doing a burst




8.2.3 SPLIT Transaction Viable Scenario

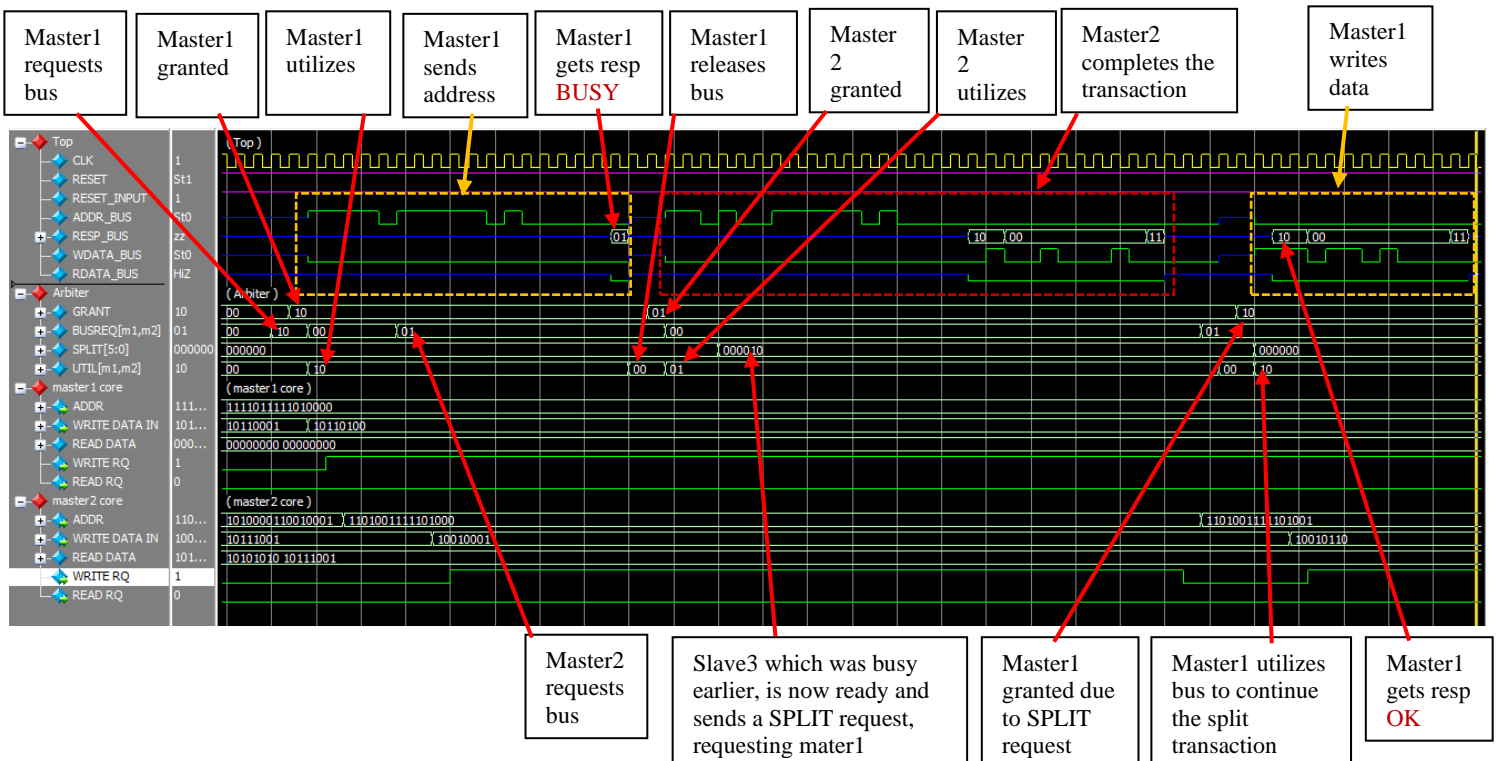


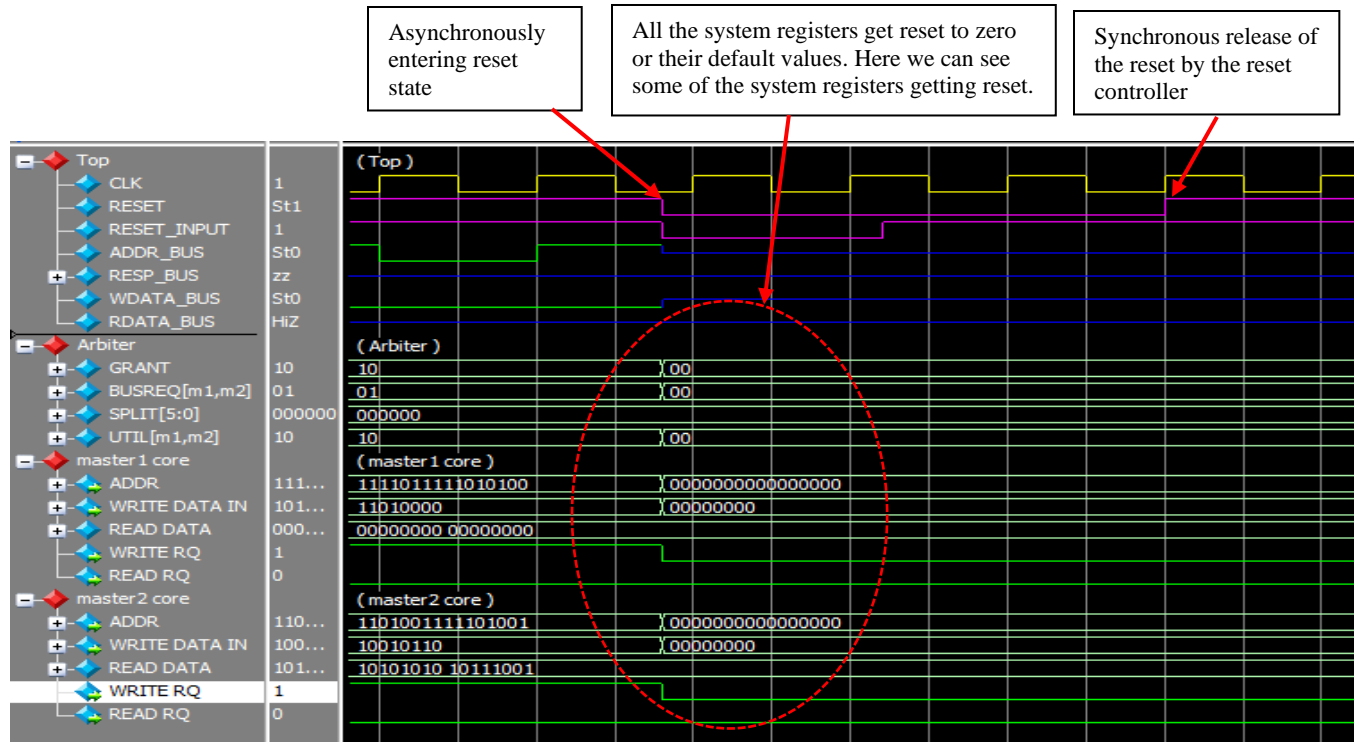8.2.4 Reset Test

Finally, while the execution sequences of the two master cores were running, a reset input was given to verify whether the whole system gets properly reset and start from the beginning.



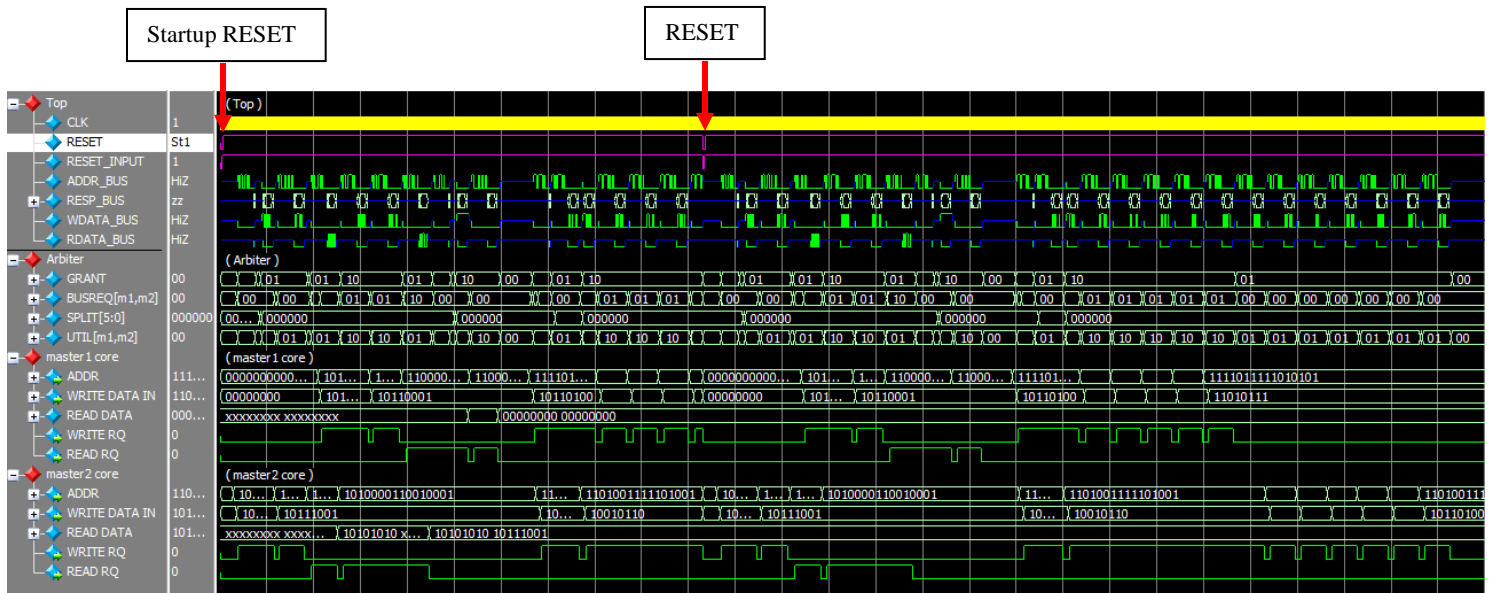Below diagram shows how all the execution sequences of two master cores repeat after reset.



9 APPENDIX

All the RTL design codes for of the completed system bus design made targeting the top-level verification are included in this section.

9.1 APPENDIX A

Top Level Testbench for top level verification. (system_bus_tb.v)

```
1  module system_bus_tb;
2
3  //Only input variables from tb to the design are clock and reset
4  reg clk      = 0;
5  reg reset    = 0;
6
7  //asynchronous reset with a 2-flop synchronizer
8  reg reset_release_ff1 = 0;
9  reg reset_release_ff2 = 0;
10 wire reset_with_synchronous_release;
11 assign reset_with_synchronous_release = reset_release_ff2 && reset;
12
13 always @(posedge clk)begin
14     reset_release_ff1 <= reset;
15     reset_release_ff2 <= reset_release_ff1;
16 end
17
18 //Initially the design is in reset state
19 initial begin
20     clk = 0;
21     #25 reset = 1; //Releasing the initial reset
22     #10281 reset = 0; //Reset test in the middle
23     #28 reset = 1; //Releasing reset in the reset test
24 end
25
26 //Clock signal generation
27 always #10 clk = ~clk;
28
29 //System Bus Instantiation
30 system_bus sb(
31     .clk      (clk),
32     .reset    (reset_with_synchronous_release)
33 );
34
35 endmodule
```

9.2 APPENDIX B

Top level module of the system bus design (system_bus.v)

```
1  module system_bus(
2      input clk,
3      input reset
4  );
5
6  //Connection wires with arbiter
7  wire [1:0] GRANT;
8  wire [1:0] BUSREQ;
```



```

9  wire [1:0] UTIL;
10 wire [5:0] GMASTER;
11 wire [5:0] SPLIT;
12
13
14 //Connection wires of the BUS
15 wire rdata_bus;
16 wire [1:0] response_bus;
17 wire addr_bus;
18 wire wdata_bus;
19
20 //Slave addresses
21 reg [1:0] slave1_addr = 2'b01;
22 reg [1:0] slave2_addr = 2'b10;
23 reg [1:0] slave3_addr = 2'b11;
24
25 //arbiter instantiation
26 arbiter a(
27     .clk (clk),
28     .reset (reset),
29     .req_from_master (BUSREQ),
30     .bus_utilization (UTIL),
31     .grant_to_master (GRANT),
32     .notify_granted_master_to_slave (GMASTER),
33     .split_req_from_slave (SPLIT)
34 );
35
36 //master1 instantiation
37 master1 m1(
38     .clk (clk),
39     .reset (reset),
40     .from_arb_grant (GRANT[1]),
41     .to_arb_req_bus (BUSREQ[1]),
42     .to_arb_bus_util (UTIL[1]),
43     .to_addr_bus (addr_bus),
44     .to_wdata_bus (wdata_bus),
45     .from_rdata_bus (rdata_bus),
46     .from_response_bus (response_bus)
47 );
48
49 //master2 instantiation
50 master2 m2(
51     .clk (clk),
52     .reset (reset),
53     .from_arb_grant (GRANT[0]),
54     .to_arb_req_bus (BUSREQ[0]),
55     .to_arb_bus_util (UTIL[0]),
56     .to_addr_bus (addr_bus),
57     .to_wdata_bus (wdata_bus),
58     .from_rdata_bus (rdata_bus),
59     .from_response_bus (response_bus)
60 );
61
62 //slave1 instantiation
63 slave_top s1(
64     .clock50 (clk),
65     .reset (reset),
66     .address_bus (addr_bus),
67     .w_data_bus (wdata_bus),
68     .r_data_bus (rdata_bus),
69     .response_bus (response_bus),
70     .split_request (SPLIT[5:4]),
71     .granted_master (GMASTER[5:4]),

```

```

72     .slave_address (slave1_addr)
73 );
74
75 //slave2 instantiation
76 slave_top s2(
77     .clock50        (clk),
78     .reset          (reset),
79     .address_bus    (addr_bus),
80     .w_data_bus     (wdata_bus),
81     .r_data_bus     (rdata_bus),
82     .response_bus   (response_bus),
83     .split_request  (SPLIT[3:2]),
84     .granted_master (GMMASTER[3:2]),
85     .slave_address  (slave2_addr)
86 );
87
88 //slave3 instantiation
89 slave_top s3(
90     .clock50        (clk),
91     .reset          (reset),
92     .address_bus    (addr_bus),
93     .w_data_bus     (wdata_bus),
94     .r_data_bus     (rdata_bus),
95     .response_bus   (response_bus),
96     .split_request  (SPLIT[1:0]),
97     .granted_master (GMMASTER[1:0]),
98     .slave_address  (slave3_addr)
99 );
100
101 endmodule

```

9.3 APPENDIX C

Master1 top module connecting master1 core module and master interface together(master1.v)

```

1  module master1(
2  input      clk,
3  input      reset,
4  input      from_arb_grant,
5  output     to_arb_req_bus,
6  output     to_arb_bus_util,
7  output tri to_addr_bus,
8  output tri to_wdata_bus,
9  input      from_rdata_bus,
10 input [1:0] from_response_bus
11 );
12
13 wire mibufin_addr;
14 wire mibufin_wdata;
15 wire mibufin_addr_en;
16 wire mibufin_wdata_en;
17
18 //Connection Wires
19 wire [15:0] mmi_addr;
20 wire        mmi_write_addr_req;
21 wire [7:0]  mmi_write_data;
22 wire        mmi_write_data_req;
23 wire        mmi_read_data_req;
24 wire        mmi_ok_response;
25 wire [7:0]  mmi_read_data;
26 wire        mmi_req_done;

```

```

27 wire          mmi_force_req;
28
29 bufif1 b_addr(to_addr_bus, mibufin_addr, mibufin_addr_en);
30 bufif1 b_wdata(to_wdata_bus, mibufin_wdata, mibufin_wdata_en);
31
32 //Master1 core instantiation
33 master1_core mcl(
34     .clk                (clk),
35     .reset              (reset),
36     .addr_to_mi         (mmi_addr),
37     .write_addr_req_to_mi (mmi_write_addr_req),
38     .write_data_to_mi   (mmi_write_data),
39     .write_data_req_to_mi (mmi_write_data_req),
40     .read_data_req_to_mi (mmi_read_data_req),
41     .ok_response_from_mi (mmi_ok_response),
42     .read_data_from_mi   (mmi_read_data),
43     .req_done_from_mi    (mmi_req_done),
44     .force_req_to_mi     (mmi_force_req)
45 );
46
47 //Master Interface instantiation for master1
48 master_interface mil(
49     .clk                (clk),
50     .reset              (reset),
51     .addr               (mibufin_addr),
52     .wdata              (mibufin_wdata),
53     .rdata              (from_rdata_bus),
54     .response            (from_response_bus),
55     .bus_req             (to_arb_req_bus),
56     .grant               (from_arb_grant),
57     .util                (to_arb_bus_util),
58
59     .addr_from_master    (mmi_addr),
60     .write_addr_req_from_master (mmi_write_addr_req),
61     .notify_ok_response_to_master (mmi_ok_response),
62     .write_data_from_master (mmi_write_data),
63     .read_data_to_master  (mmi_read_data),
64     .write_data_req_from_master (mmi_write_data_req),
65     .read_data_req_from_master (mmi_read_data_req),
66     .req_done_to_master   (mmi_req_done),
67     .force_req_from_master (mmi_force_req),
68
69     .addr_en             (mibufin_addr_en),
70     .wdata_en            (mibufin_wdata_en)
71 );
72
73 endmodule

```

9.4 APPENDIX D

Master1 core module which executes a sequence of READ, WRITE operations (master1_core.v)

```

1  module master1_core (
2      input clk,
3      input reset,
4
5      //connections with the ports of master interface to the the master side
6      //NOTE : mi - master interface
7      output reg [15:0]addr_to_mi,
8      output reg write_addr_req_to_mi = 0,
9      output reg [7:0]write_data_to_mi,

```

```

10     output reg write_data_req_to_mi = 0,
11     output reg read_data_req_to_mi = 0,
12     output reg force_req_to_mi = 0,
13     input ok_response_from_mi,
14     input [7:0] read_data_from_mi,
15     input req_done_from_mi
16 );
17
18 //Address Parameters
19 parameter STARTBIT = 1'b1;
20 parameter SLAVE1 = 2'b01, SLAVE2 = 2'b10, SLAVE3 = 2'b11;
21 parameter WRITE = 1'b1, READ = 1'b0;
22
23 /*
24 | -----|
25 |EXECUTION:
26 |Flow of execution of master 1 is a predefined set of read, write tasks and idle times.
27 |Flow starts from WRITE1 and ends with WRITE2 below, but we can customize any sequence.
28 |Below sequence has the following order,
29
30 |         INITIAL_IDLE -> WRITE1 -> READ1 -> IDLE1 -> WRITE2 -> END
31 |
32 |We can change parameters of those 4 tasks from below list of parameters.
33 |_____*/
34
35 //Execution Sequence Parameters
36 parameter INITIAL_IDLE_TIME = 8'd100;
37
38 parameter WRITE1_SLAVE      = SLAVE1;
39 parameter WRITE1_START_ADDR = 12'd500;
40 parameter WRITE1_DATA       = 8'd170;
41 parameter WRITE1_DATA_INCR  = 7;
42 parameter WRITE1_SIZE       = 4'd2;
43
44 parameter READ1_SLAVE      = SLAVE2;
45 parameter READ1_START_ADDR = 12'd400;
46 parameter READ1_SIZE       = 2'd2;
47
48 parameter IDLE1_CYCLES     = 8'd30;
49
50 parameter WRITE2_SLAVE      = SLAVE3;
51 parameter WRITE2_START_ADDR = 12'd2000;
52 parameter WRITE2_DATA       = 8'd180;
53 parameter WRITE2_DATA_INCR  = 7;
54 parameter WRITE2_SIZE       = 4'd6;
55
56
57 //Registers Needed for the Execution Sequence
58 reg [5:0] state = 5'd0;
59
60 reg [7:0] initial_idle_time = INITIAL_IDLE_TIME;
61
62 reg [11:0] writel_addr      = WRITE1_START_ADDR;
63 reg [7:0] writel_data       = WRITE1_DATA;
64 reg [3:0] writel_size       = WRITE1_SIZE;
65
66 reg [11:0] read1_addr       = READ1_START_ADDR;
67 reg [3:0] read1_size        = READ1_SIZE;
68 reg [7:0] read1_data[1:0];
69
70 reg [7:0] idle1_cycles      = IDLE1_CYCLES;
71
72 reg [11:0] write2_addr      = WRITE2_START_ADDR;

```

```

73 reg [7:0] write2_data          = WRITE2_DATA;
74 reg [3:0] write2_size          = WRITE2_SIZE;
75
76
77 /*##### STATE MACHINE #####
78 -----*/
79 //STATES:
80 parameter INITIAL_IDLE          = 0;
81
82 parameter WRITE1_UPDATE_ADDR    = 1;
83 parameter WRITE1_ADDR_RQ        = 2;
84 parameter WRITE1_OK_RES         = 3;
85 parameter WRITE1_UPDATE_DATA    = 4;
86 parameter WRITE1_DATA_RQ        = 5;
87 parameter WRITE1_RQ_DONE        = 6;
88
89 parameter READ1_UPDATE_ADDR     = 7;
90 parameter READ1_ADDR_RQ         = 8;
91 parameter READ1_OK_RES          = 9;
92 parameter READ1_DATA_RQ         = 10;
93 parameter READ1_RQ_DONE         = 11;
94
95 parameter IDLE1                 = 12;
96
97 parameter WRITE2_UPDATE_ADDR    = 13;
98 parameter WRITE2_ADDR_RQ        = 14;
99 parameter WRITE2_OK_RES         = 15;
100 parameter WRITE2_UPDATE_DATA    = 16;
101 parameter WRITE2_DATA_RQ        = 17;
102 parameter WRITE2_RQ_DONE        = 18;
103
104 parameter ALL_DONE              = 19;
105
106 //STATE MACHINE:
107 always@(posedge clk or negedge reset) begin
108     if(~reset)begin
109         addr_to_mi                <= 0;
110         write_addr_req_to_mi      <= 0;
111         write_data_to_mi          <= 0;
112         write_data_req_to_mi      <= 0;
113         read_data_req_to_mi       <= 0;
114         force_req_to_mi           <= 0;
115
116         state                     <= 5'd0;
117         initial_idle_time         <= INITIAL_IDLE_TIME;
118         writel_addr               <= WRITE1_START_ADDR;
119         writel_data               <= WRITE1_DATA;
120         writel_size               <= WRITE1_SIZE;
121         readl_addr               <= READ1_START_ADDR;
122         readl_size               <= READ1_SIZE;
123         idle1_cycles             <= IDLE1_CYCLES;
124         write2_addr              <= WRITE2_START_ADDR;
125         write2_data              <= WRITE2_DATA;
126         write2_size              <= WRITE2_SIZE;
127     end
128
129     else begin
130         case(state)
131
132             //##### INITIAL IDLE TIME #####
133             INITIAL_IDLE: begin
134                 if(initial_idle_time > 0)
135                     initial_idle_time <= initial_idle_time -1;

```

```

136         else
137             state <= WRITE1_UPDATE_ADDR;
138         end
139
140         //##### WRITE1 #####
141     WRITE1_UPDATE_ADDR: begin
142         if(writel_size == 0)begin
143             state <= READ1_UPDATE_ADDR;
144         end
145         else begin
146             force_req_to_mi <= 0;
147             writel_size <= writel_size-1;
148             addr_to_mi <= {STARTBIT, WRITE1_SLAVE, WRITE, writel_addr};
149             writel_addr <= writel_addr + 1;
150             state <= WRITE1_ADDR_RQ;
151         end
152     end
153
154     WRITE1_ADDR_RQ: begin
155         write_addr_req_to_mi <= 1;
156         state <= WRITE1_OK_RES;
157     end
158
159     WRITE1_OK_RES: begin
160         if(ok_response_from_mi == 1)begin
161             write_addr_req_to_mi <= 0;
162             state <= WRITE1_UPDATE_DATA;
163         end
164     end
165
166     WRITE1_UPDATE_DATA: begin
167         write_data_to_mi <= writel_data;
168         writel_data <= writel_data + WRITE1_DATA_INCR;
169         state <= WRITE1_DATA_RQ;
170     end
171
172     WRITE1_DATA_RQ: begin
173         write_data_req_to_mi <= 1;
174         state <= WRITE1_RQ_DONE;
175     end
176
177     WRITE1_RQ_DONE: begin
178         if(req_done_from_mi == 1) begin
179             write_data_req_to_mi <= 0;
180             state <= WRITE1_UPDATE_ADDR;
181
182             if(writel_size != 0)begin
183                 force_req_to_mi <= 1;
184             end
185         end
186     end
187
188     //##### READ1 #####
189     READ1_UPDATE_ADDR: begin
190         if(readl_size == 0)begin
191             state <= IDLE1;
192         end
193         else begin
194             force_req_to_mi <= 0;
195             readl_size <= readl_size-1;
196             addr_to_mi <= {STARTBIT, READ1_SLAVE, READ, readl_addr};
197             readl_addr <= readl_addr + 1;
198             state <= READ1_ADDR_RQ;

```

```

199         end
200     end
201
202     READ1_ADDR_RQ: begin
203         write_addr_req_to_mi <= 1;
204         state <= READ1_OK_RES;
205     end
206
207     READ1_OK_RES: begin
208         if(ok_response_from_mi == 1)begin
209             write_addr_req_to_mi <= 0;
210             state <= READ1_DATA_RQ;
211         end
212     end
213
214     READ1_DATA_RQ: begin
215         read_data_req_to_mi <= 1;
216         state <= READ1_RQ_DONE;
217     end
218
219     READ1_RQ_DONE: begin
220         if(req_done_from_mi == 1) begin
221             read_data_req_to_mi <= 0;
222             read1_data[read1_size] <= read_data_from_mi;
223             state <= READ1_UPDATE_ADDR;
224
225             if(read1_size != 0)begin
226                 force_req_to_mi <= 1;
227             end
228         end
229     end
230
231
232     //////////////////////////////////// IDLE1 ////////////////////////////////////
233     IDLE1: begin
234         if(idle1_cycles == 0) begin
235             state <= WRITE2_UPDATE_ADDR;
236         end
237         idle1_cycles <= idle1_cycles -1;
238     end
239
240
241     //////////////////////////////////// WRITE2 ////////////////////////////////////
242     WRITE2_UPDATE_ADDR: begin
243         if(write2_size == 0)begin
244             state <= ALL_DONE;
245         end
246         else begin
247             force_req_to_mi <= 0;
248             write2_size <= write2_size-1;
249             addr_to_mi <= {STARTBIT, WRITE2_SLAVE, WRITE, write2_addr};
250             write2_addr <= write2_addr + 1;
251             state <= WRITE2_ADDR_RQ;
252         end
253     end
254
255     WRITE2_ADDR_RQ: begin
256         write_addr_req_to_mi <= 1;
257         state <= WRITE2_OK_RES;
258     end
259
260     WRITE2_OK_RES: begin
261         if(ok_response_from_mi == 1)begin

```

```

262         write_addr_req_to_mi <= 0;
263         state <= WRITE2_UPDATE_DATA;
264     end
265 end
266
267 WRITE2_UPDATE_DATA: begin
268     write_data_to_mi <= write2_data;
269     write2_data <= write2_data + WRITE2_DATA_INCR;
270     state <= WRITE2_DATA_RQ;
271 end
272
273 WRITE2_DATA_RQ: begin
274     write_data_req_to_mi <= 1;
275     state <= WRITE2_RQ_DONE;
276 end
277 WRITE2_RQ_DONE: begin
278     if(req_done_from_mi == 1) begin
279         write_data_req_to_mi <= 0;
280         state <= WRITE2_UPDATE_ADDR;
281
282         if(write2_size != 0)begin
283             force_req_to_mi <= 1;
284         end
285     end
286 end
287
288
289 //##### END #####
290 ALL_DONE: begin
291     state <= ALL_DONE;
292 end
293
294 endcase
295 end
296
297 end
298
299
300 endmodule

```

9.5 APPENDIX E

Master2 top module connecting master2 core module and master interface together(master2.v)

```

1  module master2(
2  input      clk,
3  input      reset,
4  input      from_arb_grant,
5  output     to_arb_req_bus,
6  output     to_arb_bus_util,
7  output tri to_addr_bus,
8  output tri to_wdata_bus,
9  input      from_rdata_bus,
10 input [1:0]from_response_bus
11 );
12
13 wire mibufin_addr;
14 wire mibufin_wdata;
15 wire mibufin_addr_en;
16 wire mibufin_wdata_en;
17

```



```

18 //Connection Wires
19 wire [15:0] mmi_addr;
20 wire      mmi_write_addr_req;
21 wire [7:0] mmi_write_data;
22 wire      mmi_write_data_req;
23 wire      mmi_read_data_req;
24 wire      mmi_ok_response;
25 wire [7:0] mmi_read_data;
26 wire      mmi_req_done;
27 wire      mmi_force_req;
28
29 bufif1 b_addr(to_addr_bus, mibufin_addr, mibufin_addr_en);
30 bufif1 b_wdata(to_wdata_bus, mibufin_wdata, mibufin_wdata_en);
31
32 //Master2 core instantiation
33 master2_core mc2(
34     .clk                      (clk),
35     .reset                    (reset),
36     .addr_to_mi               (mmi_addr),
37     .write_addr_req_to_mi     (mmi_write_addr_req),
38     .write_data_to_mi         (mmi_write_data),
39     .write_data_req_to_mi     (mmi_write_data_req),
40     .read_data_req_to_mi      (mmi_read_data_req),
41     .ok_response_from_mi      (mmi_ok_response),
42     .read_data_from_mi        (mmi_read_data),
43     .req_done_from_mi         (mmi_req_done),
44     .force_req_to_mi          (mmi_force_req)
45 );
46
47 //Master Interface instantiation for master2
48 master_interface mi2(
49     .clk                      (clk),
50     .reset                    (reset),
51     .addr                     (mibufin_addr),
52     .wdata                     (mibufin_wdata),
53     .rdata                     (from_rdata_bus),
54     .response                  (from_response_bus),
55     .bus_req                   (to_arb_req_bus),
56     .grant                     (from_arb_grant),
57     .util                      (to_arb_bus_util),
58
59     .addr_from_master          (mmi_addr),
60     .write_addr_req_from_master (mmi_write_addr_req),
61     .notify_ok_response_to_master (mmi_ok_response),
62     .write_data_from_master     (mmi_write_data),
63     .read_data_to_master        (mmi_read_data),
64     .write_data_req_from_master (mmi_write_data_req),
65     .read_data_req_from_master  (mmi_read_data_req),
66     .req_done_to_master         (mmi_req_done),
67     .force_req_from_master      (mmi_force_req),
68
69     .addr_en                   (mibufin_addr_en),
70     .wdata_en                  (mibufin_wdata_en)
71 );
72
73 endmodule

```

9.6 APPENDIX F

Master2 core module which executes a sequence of READ, WRITE operations (master2_core.v)

```
1  module master2_core (
2      input  clk,
3      input  reset,
4
5      //connections with the ports of master interface to the the master side
6      //NOTE : mi - master interface
7      output reg [15:0]addr_to_mi,
8      output reg write_addr_req_to_mi = 0,
9      output reg [7:0]write_data_to_mi,
10     output reg write_data_req_to_mi = 0,
11     output reg read_data_req_to_mi  = 0,
12     output reg force_req_to_mi = 0,
13     input  ok_response_from_mi,
14     input [7:0]read_data_from_mi,
15     input req_done_from_mi
16 );
17
18 //Address Parameters
19 parameter STARTBIT = 1'b1;
20 parameter SLAVE1 = 2'b01, SLAVE2 = 2'b10, SLAVE3 = 2'b11;
21 parameter WRITE = 1'b1, READ = 1'b0;
22
23 /*
24 | -----|
25 |EXECUTION:
26 |Flow of execution of master 2 is a predefined set of read, write tasks and idle times.
27 |Flow starts from WRITE1 and ends with WRITE2 below, but we can customize any sequence.
28 |Below sequence has the following order,
29
30 |          INITIAL_IDLE -> WRITE1 -> READ1 -> IDLE1 -> WRITE2 -> END
31 |
32 |We can change parameters of those 4 tasks from below list of parameters.
33 | -----*/
34
35 //Execution Sequence Parameters
36 parameter INITIAL_IDLE_TIME = 8'd10;
37
38 parameter WRITE1_SLAVE      = SLAVE1;
39 parameter WRITE1_START_ADDR = 12'd400;
40 parameter WRITE1_DATA       = 8'd170;
41 parameter WRITE1_DATA_INCR  = 15;
42 parameter WRITE1_SIZE       = 4'd2;
43
44 parameter READ1_SLAVE      = SLAVE1;
45 parameter READ1_START_ADDR = 12'd400;
46 parameter READ1_SIZE       = 2'd2;
47
48 parameter IDLE1_CYCLES      = 8'd110;
49
50 parameter WRITE2_SLAVE      = SLAVE2;
51 parameter WRITE2_START_ADDR = 12'd1000;
52 parameter WRITE2_DATA       = 8'd145;
53 parameter WRITE2_DATA_INCR  = 5;
54 parameter WRITE2_SIZE       = 4'd8;
55
56
57 //Registers Needed for the Execution Sequence
58 reg [5:0] state = 5'd0;
```

```

59
60 reg [7:0]  initial_idle_time  = INITIAL_IDLE_TIME;
61
62 reg [11:0] writel_addr        = WRITE1_START_ADDR;
63 reg [7:0]  writel_data        = WRITE1_DATA;
64 reg [3:0]  writel_size        = WRITE1_SIZE;
65
66 reg [11:0] read1_addr         = READ1_START_ADDR;
67 reg [3:0]  read1_size         = READ1_SIZE;
68 reg [7:0]  read1_data[1:0];
69
70 reg [7:0]  idle1_cycles       = IDLE1_CYCLES;
71
72 reg [11:0] write2_addr        = WRITE2_START_ADDR;
73 reg [7:0]  write2_data        = WRITE2_DATA;
74 reg [3:0]  write2_size        = WRITE2_SIZE;
75
76
77 /*##### STATE MACHINE #####
78 -----*/
79 //STATES:
80 parameter INITIAL_IDLE          = 0;
81
82 parameter WRITE1_UPDATE_ADDR    = 1;
83 parameter WRITE1_ADDR_RQ        = 2;
84 parameter WRITE1_OK_RES         = 3;
85 parameter WRITE1_UPDATE_DATA    = 4;
86 parameter WRITE1_DATA_RQ        = 5;
87 parameter WRITE1_RQ_DONE        = 6;
88
89 parameter READ1_UPDATE_ADDR     = 7;
90 parameter READ1_ADDR_RQ         = 8;
91 parameter READ1_OK_RES          = 9;
92 parameter READ1_DATA_RQ         = 10;
93 parameter READ1_RQ_DONE         = 11;
94
95 parameter IDLE1                 = 12;
96
97 parameter WRITE2_UPDATE_ADDR    = 13;
98 parameter WRITE2_ADDR_RQ        = 14;
99 parameter WRITE2_OK_RES         = 15;
100 parameter WRITE2_UPDATE_DATA    = 16;
101 parameter WRITE2_DATA_RQ        = 17;
102 parameter WRITE2_RQ_DONE        = 18;
103
104 parameter ALL_DONE              = 19;
105
106 //STATE MACHINE:
107 always@(posedge clk or negedge reset) begin
108     if(~reset)begin
109         addr_to_mi             <= 0;
110         write_addr_req_to_mi    <= 0;
111         write_data_to_mi       <= 0;
112         write_data_req_to_mi    <= 0;
113         read_data_req_to_mi     <= 0;
114         force_req_to_mi        <= 0;
115
116         state                   <= 5'd0;
117         initial_idle_time       <= INITIAL_IDLE_TIME;
118         writel_addr             <= WRITE1_START_ADDR;
119         writel_data             <= WRITE1_DATA;
120         writel_size             <= WRITE1_SIZE;
121         read1_addr             <= READ1_START_ADDR;

```

```

122     read1_size           <= READ1_SIZE;
123     idle1_cycles        <= IDLE1_CYCLES;
124     write2_addr         <= WRITE2_START_ADDR;
125     write2_data         <= WRITE2_DATA;
126     write2_size         <= WRITE2_SIZE;
127 end
128
129 else begin
130     case(state)
131
132         //##### INITIAL IDLE TIME #####
133         INITIAL_IDLE: begin
134             if(initial_idle_time > 0)
135                 initial_idle_time <= initial_idle_time -1;
136             else
137                 state <= WRITE1_UPDATE_ADDR;
138             end
139         end
140
141         //##### WRITE1 #####
142         WRITE1_UPDATE_ADDR: begin
143             if(writel_size == 0)begin
144                 state <= READ1_UPDATE_ADDR;
145             end
146             else begin
147                 force_req_to_mi <= 0;
148                 writel_size <= writel_size-1;
149                 addr_to_mi <= {STARTBIT, WRITE1_SLAVE, WRITE, writel_addr};
150                 writel_addr <= writel_addr + 1;
151                 state <= WRITE1_ADDR_RQ;
152             end
153         end
154
155         WRITE1_ADDR_RQ: begin
156             write_addr_req_to_mi <= 1;
157             state <= WRITE1_OK_RES;
158         end
159
160         WRITE1_OK_RES: begin
161             if(ok_response_from_mi == 1)begin
162                 write_addr_req_to_mi <= 0;
163                 state <= WRITE1_UPDATE_DATA;
164             end
165         end
166
167         WRITE1_UPDATE_DATA: begin
168             write_data_to_mi <= writel_data;
169             writel_data <= writel_data + WRITE1_DATA_INCR;
170             state <= WRITE1_DATA_RQ;
171         end
172
173         WRITE1_DATA_RQ: begin
174             write_data_req_to_mi <= 1;
175             state <= WRITE1_RQ_DONE;
176         end
177
178         WRITE1_RQ_DONE: begin
179             if(req_done_from_mi == 1) begin
180                 write_data_req_to_mi <= 0;
181                 state <= WRITE1_UPDATE_ADDR;
182
183                 if(writel_size != 0)begin
184                     force_req_to_mi <= 1;
185                 end
186             end
187         end
188     end

```

```

185         end
186
187
188         //##### READ1 #####
189         READ1_UPDATE_ADDR: begin
190             if(read1_size == 0)begin
191                 state <= IDLE1;
192             end
193             else begin
194                 force_req_to_mi <= 0;
195                 read1_size <= read1_size-1;
196                 addr_to_mi <= {STARTBIT, READ1_SLAVE, READ, read1_addr};
197                 read1_addr <= read1_addr + 1;
198                 state <= READ1_ADDR_RQ;
199             end
200         end
201
202         READ1_ADDR_RQ: begin
203             write_addr_req_to_mi <= 1;
204             state <= READ1_OK_RES;
205         end
206
207         READ1_OK_RES: begin
208             if(ok_response_from_mi == 1)begin
209                 write_addr_req_to_mi <= 0;
210                 state <= READ1_DATA_RQ;
211             end
212         end
213
214         READ1_DATA_RQ: begin
215             read_data_req_to_mi <= 1;
216             state <= READ1_RQ_DONE;
217         end
218
219         READ1_RQ_DONE: begin
220             if(req_done_from_mi == 1) begin
221                 read_data_req_to_mi <= 0;
222                 read1_data[read1_size] <= read_data_from_mi;
223                 state <= READ1_UPDATE_ADDR;
224
225                 if(read1_size != 0)begin
226                     force_req_to_mi <= 1;
227                 end
228             end
229         end
230
231
232         //##### IDLE1 #####
233         IDLE1: begin
234             if(idle1_cycles == 0) begin
235                 state <= WRITE2_UPDATE_ADDR;
236             end
237             idle1_cycles <= idle1_cycles -1;
238         end
239
240
241         //##### WRITE2 #####
242         WRITE2_UPDATE_ADDR: begin
243             if(write2_size == 0)begin
244                 state <= ALL_DONE;
245             end
246             else begin
247                 force_req_to_mi <= 0;

```

```

248         write2_size <= write2_size-1;
249         addr_to_mi <= {STARTBIT, WRITE2_SLAVE, WRITE, write2_addr};
250         write2_addr <= write2_addr + 1;
251         state <= WRITE2_ADDR_RQ;
252     end
253 end
254
255 WRITE2_ADDR_RQ: begin
256     write_addr_req_to_mi <= 1;
257     state <= WRITE2_OK_RES;
258 end
259
260 WRITE2_OK_RES: begin
261     if(ok_response_from_mi == 1)begin
262         write_addr_req_to_mi <= 0;
263         state <= WRITE2_UPDATE_DATA;
264     end
265 end
266
267 WRITE2_UPDATE_DATA: begin
268     write_data_to_mi <= write2_data;
269     write2_data <= write2_data + WRITE2_DATA_INCR;
270     state <= WRITE2_DATA_RQ;
271 end
272
273 WRITE2_DATA_RQ: begin
274     write_data_req_to_mi <= 1;
275     state <= WRITE2_RQ_DONE;
276 end
277 WRITE2_RQ_DONE: begin
278     if(req_done_from_mi == 1) begin
279         write_data_req_to_mi <= 0;
280         state <= WRITE2_UPDATE_ADDR;
281
282         if(write2_size != 0)begin
283             force_req_to_mi <= 1;
284         end
285     end
286 end
287
288
289 //##### END #####
290 ALL_DONE: begin
291     state <= ALL_DONE;
292 end
293
294 endcase
295 end
296
297 end
298
299 endmodule

```

9.7 APPENDIX G

Master interface module (master_interface.v)

```
1  module master_interface(clk,
2      reset,
3      addr,
4      wdata,
5      rdata,
6      response,
7      bus_req,
8      grant,
9      util,
10
11      addr_from_master,
12      write_addr_req_from_master,
13      notify_ok_response_to_master,
14      write_data_from_master,
15      read_data_to_master,
16      write_data_req_from_master,
17      read_data_req_from_master,
18      req_done_to_master,
19      force_req_from_master,
20
21      addr_en,
22      wdata_en
23 );
24 //INPUTS &OUTPUTS:
25 // from and to the design
26 input clk;                // clock signal
27 input reset;              // reset signal
28 output addr;              //address bus
29 output wdata;             // data write bus
30 input rdata;              // data read bus
31 input [1:0] response;     // response bus from slave
32 output reg bus_req = 0;   // request to arbiter
33 input grant;              // grant permission from arbiter
34 output reg util = 0;      // utilized flag of master
35 output reg addr_en = 0;   // enable tristate buffer to addr bus
36 output reg wdata_en = 0;  // enable tristate buffer to wdata bus
37
38 //from master module
39 input [15:0] addr_from_master; //address to write to addr bus
40 input write_addr_req_from_master; // address write request
41 output reg notify_ok_response_to_master = 0;
42 input [7:0] write_data_from_master; // data to WDATA bus
43 output reg [7:0] read_data_to_master = 0; // data from RDATA bus
44 input write_data_req_from_master; // data write command
45 input read_data_req_from_master; // data read command
46 output reg req_done_to_master = 0;
47 input force_req_from_master;
48
49 // states of state machine
50 parameter IDLE = 4'b0000;
51 parameter REQUEST_BUS = 4'b0001;
52 parameter SENDADDRESS = 4'b0010;
53 parameter READDATA = 4'b0011;
54 parameter WRITEDATA = 4'b0100;
55 parameter SPLIT = 4'b0101;
56 parameter WAIT_FOR_SPLIT = 4'b0110;
57 parameter CHECK_NEXT = 4'b0111;
58 parameter CHECK_NEXT2 = 4'b1000;
```

```

59
60 //responses from slave
61 parameter OK = 2'b10, BUSY = 2'b01, DONE = 2'b11, NCK = 2'b00;
62
63 //internal registers
64 reg [3:0] state = IDLE;
65 reg [1:0] burst_check_cycles = 2;
66 reg [15:0] serial_slave_address;
67 reg [7:0] serial_slave_data;
68
69 //send values to address and data buses
70 assign addr = serial_slave_address[15];
71 assign wdata = serial_slave_data[7];
72
73 //STATE MACHINE:
74 always @(posedge clk or negedge reset)
75 begin
76     if(~reset) // resetting signals and registers
77     begin
78         state <= IDLE;
79         bus_req <= 0;
80         util <= 0;
81         addr_en <= 0;
82         wdata_en <= 0;
83         notify_ok_response_to_master <= 0;
84         read_data_to_master <= 0;
85         req_done_to_master <= 0;
86         serial_slave_address <= 0;
87         serial_slave_data <= 0;
88         burst_check_cycles <= 2;
89     end
90     else begin
91         case(state)
92             IDLE:begin // idle state
93                 util <= 0;
94                 addr_en <= 0;
95                 wdata_en <= 0;
96                 notify_ok_response_to_master <= 0;
97                 read_data_to_master <= 0;
98                 serial_slave_address <= 0;
99                 serial_slave_data <= 0;
100                 burst_check_cycles <= 2;
101                 /*check for a request from master core to write an address*/
102                 if(write_addr_req_from_master) begin
103                     state <= REQUEST_BUS; //go to next state if req received
104                     req_done_to_master <= 1'b0;
105                 end
106             end
107
108             REQUEST_BUS:begin //requesting bus from arbiter
109                 bus_req <= 1'b1;
110                 serial_slave_address <= addr_from_master;
111                 notify_ok_response_to_master <= 1'b1;
112                 if(grant)begin //if granted, go to next state
113                     state <= SENDADDRESS;
114                     addr_en <= 1;
115                     wdata_en <= 1;
116                     util <= 1; //make utilized flag high
117                     bus_req <= 0;
118                 end
119                 else begin //else wait in the same state
120                     state <= REQUEST_BUS;
121                 end

```



```

122     end
123
124 SENDADDRESS:begin // sending address
125     notify_ok_response_to_master <= 1'b0;
126
127     //check for OK response from slave
128     if(write_data_req_from_master && response == OK)
129     begin
130         state <= WRITEDATA; // go to write data state
131         serial_slave_data <= write_data_from_master;
132     end
133     else if(read_data_req_from_master && response == OK) begin
134         state <= READDATA; // go to read data state
135     end
136     else if(response == BUSY) begin //if slave BUSY
137         state <= WAIT_FOR_SPLIT; //go to split state
138         serial_slave_data <= write_data_from_master;
139         util <= 1'b0; //release bus utilization
140         addr_en <= 0;
141         wdata_en <= 0;
142     end
143     else begin
144         state <= SENDADDRESS;
145         //send the address serially
146         serial_slave_address[15:0] <= {serial_slave_address[14:0],1'b0};
147     end
148 end
149
150 READDATA:begin //read data state
151     if(response == DONE) begin //if slave completed sending data
152         state <= CHECK_NEXT;
153         req_done_to_master <= 1; //notify master core about completion
154     end
155     else begin
156         state <= READDATA;
157         //read data from data bus serially
158         read_data_to_master[7:0] <= {read_data_to_master[6:0],rdata};
159     end
160 end
161
162 WRITEDATA:begin //write data state
163     if(response == DONE) begin //if slave responds completion
164         state <= CHECK_NEXT;
165         req_done_to_master <= 1; //notify master core about completion
166     end
167     else begin
168         state <= WRITEDATA;
169         //write data to data bus serially
170         serial_slave_data[7:0] <= {serial_slave_data[6:0],1'b0};
171     end
172 end
173
174 WAIT_FOR_SPLIT: begin //intermediate state to pass 1 clk cycle
175     state <= SPLIT;
176 end
177
178
179 SPLIT:begin //split transaction state
180     if(grant)begin //once grant is given back
181         util <= 1'b1; //make the util line high
182         addr_en <= 1;
183         wdata_en <= 1;
184     end

```

```

185         //if OK response received and having a WRITE req, go to write state
186         if(write_data_req_from_master && response == OK && grant) begin
187             state <= WRITEDATA;
188         end
189         //if OK response received and having a READ req, go to read state
190         else if(read_data_req_from_master && response == OK && grant) begin
191             state <= READDATA;
192         end
193         else begin
194             state <= SPLIT;
195         end
196     end
197
198     CHECK_NEXT: begin
199         state <= CHECK_NEXT2;
200         if(force_req_from_master == 1)begin
201             bus_req <= 1;
202         end
203     end
204
205     CHECK_NEXT2: begin
206         state <= IDLE;
207         if(force_req_from_master == 1)begin
208             bus_req <= 1;
209         end
210     end
211
212     endcase
213 end
214 end
215 endmodule

```

9.8 APPENDIX H

Slave top module connecting slave interface with a 4K RAM module (**slave_top.v**)

```

1  module slave_top(
2
3      input wire clock50,
4      input wire reset,
5      input wire address_bus,
6      input wire w_data_bus,
7      output tri r_data_bus,
8      output tri [1:0] response_bus,
9      output wire [1:0] split_request,
10     input wire [1:0] granted_master,
11     input wire [1:0] slave_address
12 );
13 //-----WIRES-----//
14 wire [7:0]q;
15 wire [11:0]ram_address;
16 wire [7:0]ram_data;
17 wire wr_en;
18 wire sibufin_r_data_bus;
19 wire [1:0] sibufin_response_bus;
20 wire sibufin_en;
21
22 //-----Trisate Buffers for RDATA,RESPONSE bus-----//
23 bufif1 buf_r_data_bus(r_data_bus, sibufin_r_data_bus, sibufin_en);
24 bufif1 buf_response_bus1(response_bus[1], sibufin_response_bus[1], sibufin_en);
25 bufif1 buf_response_bus0(response_bus[0], sibufin_response_bus[0], sibufin_en);

```

```

26
27 //-----SLAVE_INTERFACE INSTANTIATION-----//
28 slave_interface SLAVE(
29     .clk          (clock50),
30     .reset        (reset),
31     .addr         (address_bus),
32     .w_data       (w_data_bus),
33     .r_data       (sibufin_r_data_bus),
34     .response     (sibufin_response_bus),
35     .split_request (split_request),
36     .slave_address (slave_address),
37     .granted_master (granted_master),
38     .q            (q),
39     .ram_address  (ram_address),
40     .ram_data     (ram_data),
41     .wr_en       (wr_en),
42     .slave_en     (sibufin_en)
43 );
44
45 //-----RAM_INSTANCE-----//
46 syncRAM RAM_BASIC(
47     .dataOut      (q),
48     .dataIn       (ram_data),
49     .Clk          (clock50),
50     .Addr         (ram_address),
51     .Wr_en       (wr_en),
52     .reset        (reset)
53 );
54 endmodule

```

9.9 APPENDIX I

Slave interface with address decoder (**slave_interface.v**)

```

1  module slave_interface(
2
3      input wire clk,      //system clock input
4      input wire reset,   //active low reset
5      input wire addr,    //address bus
6      input wire w_data,  //write data bus
7      output wire r_data, //read data bus
8      output [1:0] response, //response bus
9      output [1:0] split_request, //request split transaction
10     input  [1:0] granted_master, //indicates the active master on the bus
11     input wire [1:0] slave_address, //sets the device address of the slave
12     output reg slave_en, // enable signal for tri-state buffers
13
14     //-----for ram-----//
15     input wire [7:0] q, // output data from the ram
16     output [11:0] ram_address, //address input of the ram
17     output [7:0] ram_data, // data input to the ram
18     output wr_en
19 );
20 //-----PARAMETERS-----//
21 //---STATES---//
22 parameter AWAITING_GRANT = 4'b0000;
23 parameter START_BIT = 4'b0001;
24 parameter GET_ADDR = 4'b0010;
25 parameter SEND_RESPONSE_ADDRESS = 4'b0011 ;
26 parameter GET_DATA = 4'b0100 ;
27 parameter SEND_DATA = 4'b0101 ;

```

```

28 parameter SEND_RESPONSE_DATA = 4'b0110 ;
29 parameter SPLIT = 4'b0111;
30 parameter WAIT_BEFORE_GET_DATA = 4'b1000;
31 //---RESPONSES---//
32 parameter RESP_NAK = 2'b00;
33 parameter RESP_BUSY=2'b01;
34 parameter RESP_OK  =2'b10;
35 parameter RESP_DONE=2'b11;
36
37 //-----REGISTERS-----//
38 reg [3:0] state      = START_BIT;
39
40 reg [15:0]r_addr      =0;
41 reg [7:0]r_data_in    =0;
42 reg r_data_out        =0;
43 reg [1:0]r_response   =0;
44 reg [1:0]r_split      =0;
45 reg [4:0]addr_count   =0;
46 reg [3:0]data_count   =0;
47 reg wr_en_bit         =0;
48 reg [15:0]split_adress =0;
49 reg [1:0]split_master =0;
50 reg [1:0]r_split_request=0;
51 reg [3:0]busy_count   =5;
52
53
54 //-----STATE_MACHINE-----//
55
56 always @ (posedge clk or negedge reset) begin
57     // This is a active low asynchronous reset.
58     // This will reset all the registers to their default state.
59     if (~reset) begin
60         state <= START_BIT;
61         wr_en_bit<=0;
62         r_addr<=0;
63         r_data_in<=0;
64         r_data_out<=0;
65         r_response<=RESP_NAK;
66         r_split<=0;
67         addr_count<=0;
68         data_count<=0;
69         busy_count<=5;
70         slave_en <=0;
71         split_adress <= 0;
72         split_master <= 0;
73         r_split_request <= 0;
74     end else begin
75
76         case (state)
77             // This is the default state of the module
78             // This states ideintifies the start bit of the address
79             START_BIT: begin
80                 slave_en <= 0;
81                 if (addr==1) begin
82                     state <= GET_ADDR;
83                     addr_count<=14;
84                     wr_en_bit<=0;
85                     r_addr<=0;
86                     r_data_in<=0;
87                     r_data_out<=0;
88                 end
89             else
90                 state <= START_BIT;

```

```

91
92     addr_count<=15;
93     r_response<=RESP_NAK;
94 end
95 //Capturs the 15-bit address which follows the start bit
96 GET_ADDR: begin
97
98     if (addr_count>1) begin
99         r_addr[15:0] <= {r_addr[14:0],addr};
100         addr_count <= addr_count -1;
101         state <= GET_ADDR;
102     end else begin
103         r_addr[15:0] <= {r_addr[14:0],addr};
104         state <= SEND_RESPONSE_ADDRESS;
105     end
106     wr_en_bit<=0;
107     r_response<=RESP_NAK;
108 end
109
110 //decode the slave address and the type of transaction (mem r/w)
111 //and send the appropriate response to the master.
112 SEND_RESPONSE_ADDRESS: begin
113
114     if (r_addr[14:13] == slave_address) begin //check for slave address
115         slave_en <= 1;
116
117         if(busy_count == 0)begin
118             if (r_addr[12]==1) begin // do this for mem write
119                 state<= WAIT_BEFORE_GET_DATA;
120                 r_response<=RESP_OK;
121                 data_count<=8;
122             end
123             else begin // do this for mem read
124                 state<= SEND_DATA;
125                 r_response<=RESP_OK;
126                 data_count<=7;
127             end
128         end
129         else begin
130             r_response<=RESP_BUSY; // send BUSY response
131             split_address<= r_addr;
132             split_master<= granted_master;
133             state <= SPLIT;
134         end
135     end
136     else begin
137         state<=START_BIT;
138     end
139 end
140
141 // captures the 8bit data which is to be written to the ram
142 GET_DATA: begin
143     if (data_count>1) begin
144         r_data_in[7:0]<= {r_data_in[6:0],w_data};
145         data_count<=data_count-1;
146         state<=GET_DATA;
147     end else begin
148         r_data_in[7:0]<= {r_data_in[6:0],w_data};
149         state <= SEND_RESPONSE_DATA;
150         wr_en_bit<=1;
151     end
152     r_response<=RESP_NAK;
153 end

```

```

154
155 // send the data from the ram to the master
156 SEND_DATA: begin
157     if (data_count>0) begin
158         r_data_out<= q[data_count];
159         data_count<=data_count-1;
160         state<=SEND_DATA;
161     end else begin
162         r_data_out<= q[data_count];
163         state <= SEND_RESPONSE_DATA;
164         wr_en_bit<=0;
165     end
166     r_response<=RESP_NAK;
167 end
168 // send the DONE sesponse to the master which indicates
169 // a successfull data transfer.
170 SEND_RESPONSE_DATA: begin
171     wr_en_bit<=0;
172     r_response<=RESP_DONE;
173     state <=START_BIT;
174 end
175 // comes here after sending a BUSY response
176 // waits until the slave is ready.
177 SPLIT: begin
178     slave_en <= 0;
179     if (busy_count != 0) begin
180         busy_count<=busy_count-1;
181     end
182     else begin
183         r_split_request<=split_master;
184         state <= AWATING_GRANT;
185     end
186 end
187
188 // after requesting a split transaction wait here until the
189 // arbiter grants permission
190 AWATING_GRANT: begin
191     if (granted_master==split_master) begin
192         r_addr<=split_address;
193         state<= SEND_RESPONSE_ADDRESS;
194         r_split_request<=0;
195     end else begin
196         state <= AWATING_GRANT;
197     end
198 end
199 // wait one clock cycle before capture data
200 WAIT_BEFORE_GET_DATA: begin
201     state<=GET_DATA;
202 end
203 endcase // state
204
205 end
206
207 end
208 assign response = r_response;
209 assign ram_address = r_addr[11:0];
210 assign ram_data = r_data_in;
211 assign wr_en =wr_en_bit;
212 assign r_data=r_data_out;
213 assign split_request=r_split_request;
214 endmodule

```

9.10 APPENDIX J

RAM module connected to slave interface (**syncRAM.v**)

```
1  module syncRAM( dataIn,
2                  dataOut,
3                  Addr,
4                  Wr_en,
5                  Clk,
6                  reset
7  );
8
9
10 // parameters for the width
11 parameter ADR    = 12;
12 parameter DAT    = 8;
13 parameter DPTH   = 4096;
14
15 //ports
16 input    [DAT-1:0] dataIn;
17 output reg [DAT-1:0] dataOut;
18 input    [ADR-1:0] Addr;
19 input                    Wr_en, Clk, reset;
20
21 //internal variables
22 integer i;
23 reg [DAT-1:0] SRAM [DPTH-1:0];
24
25 always @ (posedge Clk or negedge reset)
26 begin
27     if(~reset)begin
28         for (i=0; i<DPTH; i=i+1) SRAM[i] <= 0;
29     end
30     else begin
31         if (Wr_en == 1'b1 ) begin
32             SRAM [Addr] <= dataIn;
33         end
34
35         else begin
36             dataOut <= SRAM [Addr];
37         end
38     end
39 end
40
41 endmodule
```

9.11 APPENDIX K

Arbiter code (**arbiter.v**)

```
1  module arbiter (
2      input clk,
3      input reset,
4      input [1:0]req_from_master,    //BUSREQ signals in format:[m1,m2]
5
6      //SPLIT signals in format:[s1->m1,s1->m2,s2->m1,s2->m2,s3->m1,s3->m2]
7      input [5:0]split_req_from_slave,
8
9      input [1:0]bus_utilization,    //UTIL signals in format:[m1,m2]
10     output reg [1:0]grant_to_master, //GRANT signals in format:[m1,m2]
```

```


11
12     //GMASTER signals in format:[s1<-m1,s1<-m2,s2<-m1,s2<-m2,s3<-m1,s3<-m2]
13     output reg [5:0]notify_granted_master_to_slave
14 );
15
16 wire [1:0]current_requests;//[m1 requested?, m2 requested ?]
17
18 /*either get responses from masters or get request from slaves waiting in
19 the split states to grant permission for corresponding master*/
20 assign current_requests[1] = req_from_master[1] || split_req_from_slave[5]
21     || split_req_from_slave[3] || split_req_from_slave[1];
22 assign current_requests[0] = req_from_master[0] || split_req_from_slave[4]
23     || split_req_from_slave[2] || split_req_from_slave[0];
24
25 // initially no master is granted. no master is notified to slave
26 initial begin
27     grant_to_master                <= 2'b00;
28     notify_granted_master_to_slave <= 6'b000000;
29 end
30
31 always @(posedge clk or negedge reset) begin
32     //asynchronous reset
33     if(~reset)begin
34         //reset to no grants and no granted notifications
35         grant_to_master                <= 2'b00;
36         notify_granted_master_to_slave <= 6'b000000;
37     end
38
39     //bus requests are checked and granted only when bus is not utilized
40     else if(bus_utilization == 2'b00) begin
41         case(current_requests) //process the requests from masters and slaves
42             2'b00:begin        //no requests
43                 grant_to_master                <= 2'b00;
44                 notify_granted_master_to_slave <= 6'b000000;
45             end
46             2'b10:begin        //request to grant master 1
47                 //grant master 1
48                 grant_to_master                <= 2'b10;
49                 //notify 3 slaves that master 1 is granted
50                 notify_granted_master_to_slave <= 6'b101010;
51             end
52             2'b01:begin        //request to grant master 2
53                 //grant master 2
54                 grant_to_master                <= 2'b01;
55                 //notify 3 slaves that master 2 is granted
56                 notify_granted_master_to_slave <= 6'b010101;
57             end
58             //high priority goes to master 1
59             2'b11:begin        //request to grant both master 1 and 2
60                 //master 1 is granted (high priority)
61                 grant_to_master                <= 2'b10;
62                 //notify 3 slaves that master 1 is granted
63                 notify_granted_master_to_slave <= 6'b101010;
64             end
65         endcase
66     end
67 end
68
69 endmodule

```



9.12 APPENDIX L

RTL View of the Design from Quartus


Top Level

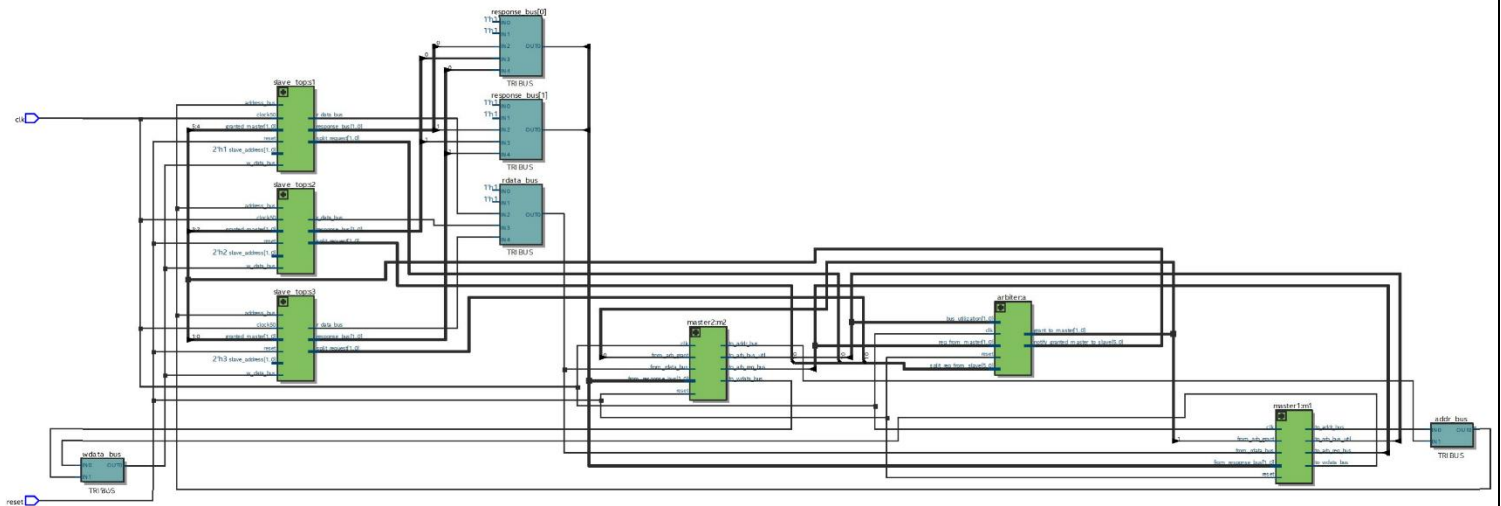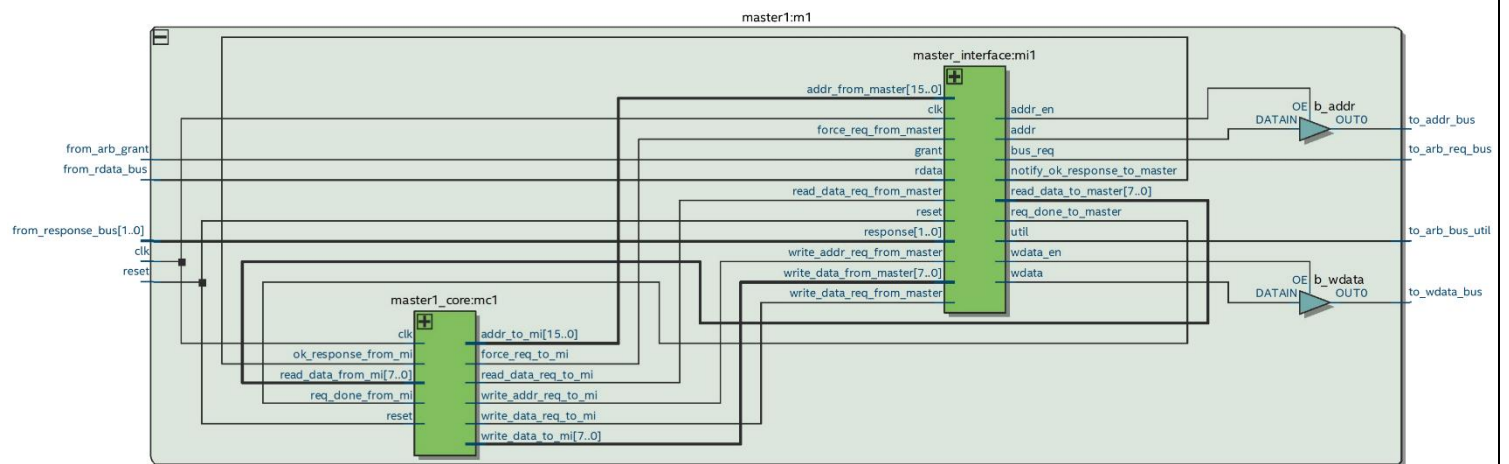

Inside a Master



Inside a Slave

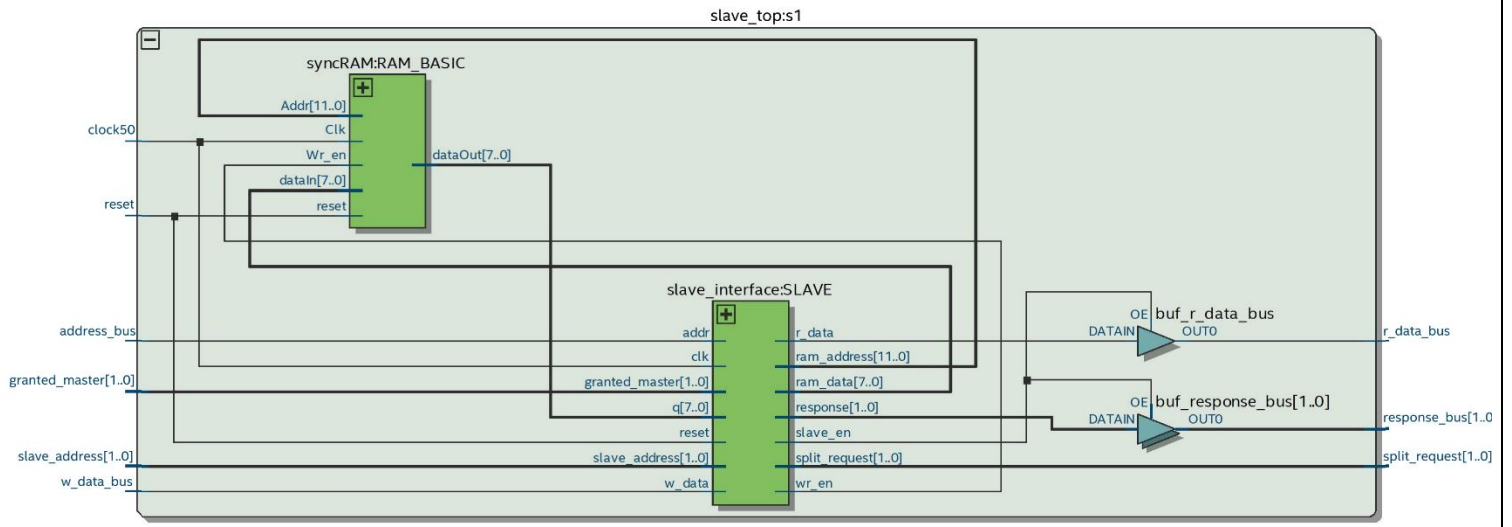

Inside Arbiter

